

CE211-L Circuit Analysis Lab



Lab Report # 10

Submitted By:

Muhammad Ayaan Asad – 2024359

Abdullah Mir – 2024041

Muhammad Haider – 2024384


Submitted to: **Engr. Muhammad Shakaib**

Semester: **03**


Faculty of Computer Science and Engineering
GIK Institute of Engineering Sciences and Technology

Task Statement:

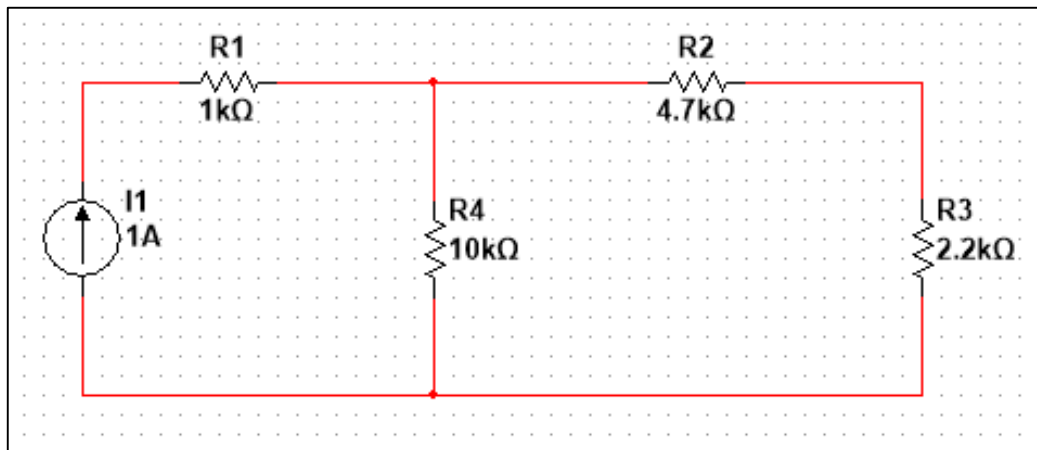1. Calculate the current (I_N) and resistance (R_{th}) in the given circuit.



Solution

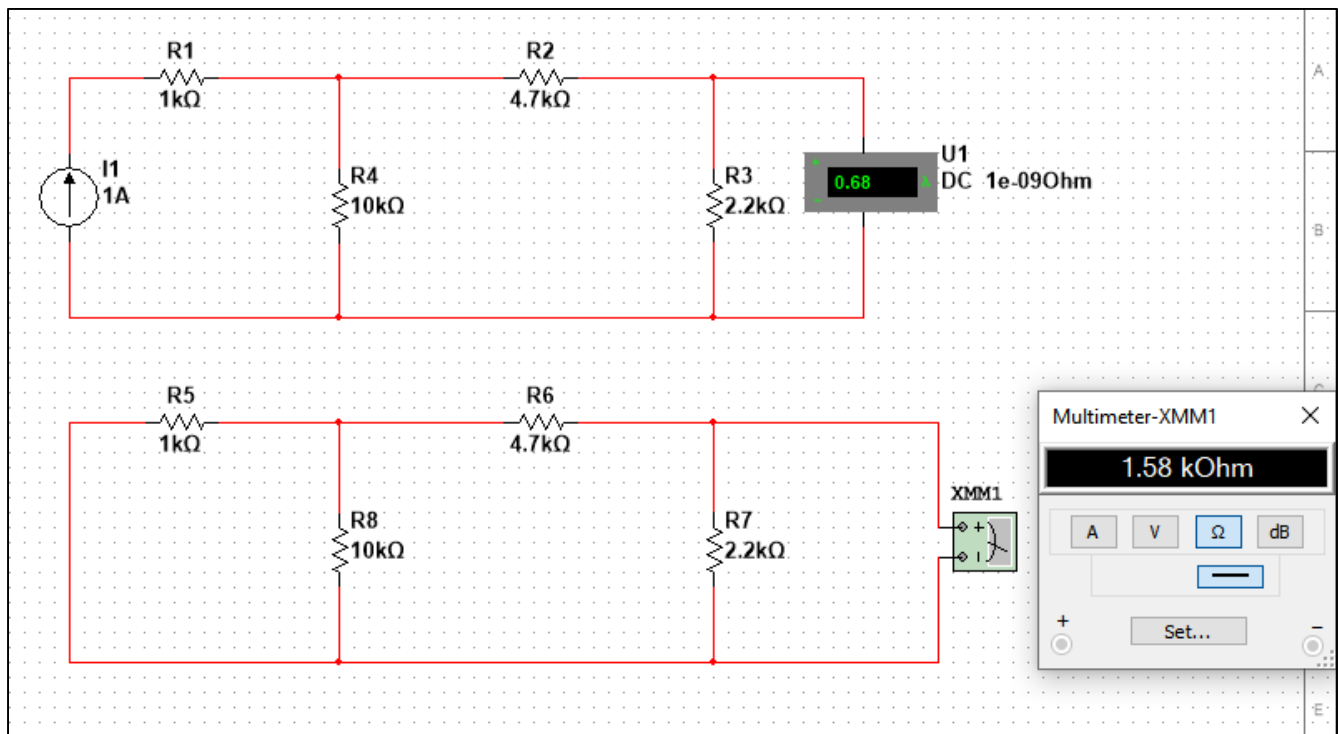

Apply Mesh Analysis:

$$I_1 = 1\text{ A}$$

KVL on Loop 2:

$$10\text{k}(I_2 - I_1) + 4.7\text{k}(I_2) + 2.2\text{k}(I_2 - I_3) = 0$$

$$-10\text{k } I_1 + 16.9\text{k } I_2 - 2.2\text{k } I_3 = 0$$

$$16.9\text{k } I_2 - 2.2\text{k } I_3 = 10\text{k} - \textbf{(1)}$$

KVL on Loop 3:

$$2.2\text{k } (I_3 - I_2) = 0$$

$$2.2\text{k } I_3 - 2.2\text{k } I_2 = 0 - \textbf{(2)}$$

$$I_2 = 0.68 \text{ A}$$

$$I_3 = 0.68 \text{ A}$$

$$I_N = I_3 = 0.68 \text{ A}$$

$$R_{1\text{k} \parallel 10\text{k}} = 0.90 \text{ k}\Omega$$

$$R_{\text{series}} = 5.6 \text{ k}\Omega$$

$$R_{5.6\text{k} \parallel 2.2\text{k}} = 1.58 \text{ k}\Omega$$

$$I_N = 0.68 \text{ A}$$
$$R_{TH} = 1.58 \text{ k}\Omega$$