

Circuit Analysis

Date: _____

- A node is the junction of two or more branches.
- A branch is any portion of a circuit with two terminals connected to it.
→ In analysis, all wires that are directly connected (with no components in between) belong to the same node because they are at the same electrical potential (voltage).
In essence, a branch represents a single element such as a voltage source or a resistor.
- Two or more elements are in series if they exclusively share a single node and consequently carry the same current.
- Two or more elements are in parallel if they ~~have~~ are connected to the same two nodes and consequently have the same voltage across them.

Q. The charge entering the positive terminal of an element is $q = 5 \sin(4\pi t)$ mc while the voltage across the element (plus to minus) is $V = 3 \cos(4\pi t)$ V.

- Find the power supplied to the element at $t = 0.3$ s.
- Calculate the energy delivered to the element between 0 and 0.6 s.

$$(a) i(t) = \frac{dq}{dt}; i(t) = 4\pi(5) \cos(4\pi t) = 20\pi \cos(4\pi t) \text{ A}$$

$$\therefore \text{Power} = VI = (3 \cos(4\pi t))(20\pi \cos(4\pi t)) \\ = 60\pi \cos^2(4\pi t) \text{ mW}$$

$$\Rightarrow \text{Power @ } t = 0.3 \text{ s} = 60\pi \cos^2(4\pi(0.3)) = \underline{\underline{123.372 \text{ mW}}}$$

(b) Power tells us the energy transferred per second.

\Rightarrow Power is the rate at which work is done.

$$\therefore P = \frac{dW}{dt} ; dW = P dt$$

$$\Rightarrow \int dW = \int P dt ; W = \int_0^{0.6} P dt$$

$$\Rightarrow W = \int_0^{0.6} 60\pi \cos^2(4\pi t) dt = 60\pi \int_0^{0.6} \cos^2(4\pi t) dt$$

✓
energy delivered

$$\therefore W = 60\pi (0.31169)$$

$$W = 58.75 \text{ mJ}$$

$$\text{Let } u = 4\pi t ; du = 4\pi dt$$

$$\Rightarrow \frac{1}{4\pi} \int \cos^2(u) du$$

\Rightarrow Applying reduction formula;

$$\Rightarrow \int \cos^n(u) du = \frac{\cos^{n-1}(u) \sin(u)}{n}$$

$$+ \frac{n-1}{n} \int \cos^{n-2}(u) du$$

$$\Rightarrow \frac{\cos(u) \sin(u)}{2} + \frac{1}{2} \int 1 du$$

$$\Rightarrow \left[\frac{\cos(u) \sin(u)}{2} + \frac{u}{2} \right] \times \frac{1}{4\pi}$$

$$\Rightarrow \frac{\cos(u) \sin(u)}{8\pi} + \frac{u}{8\pi}$$

$$\Rightarrow \frac{\cos(4\pi x) \sin(4\pi x)}{8\pi} + \frac{x}{2} + C$$


$$\left[\frac{\cos(4\pi x) \sin(4\pi x)}{8\pi} + \frac{x}{2} \right]_0^{0.6}$$

$$\Rightarrow 0.31169$$

Real current source \rightarrow Small internal resistance connected in series with the source

Date: _____

Q. Find the current I_o :-

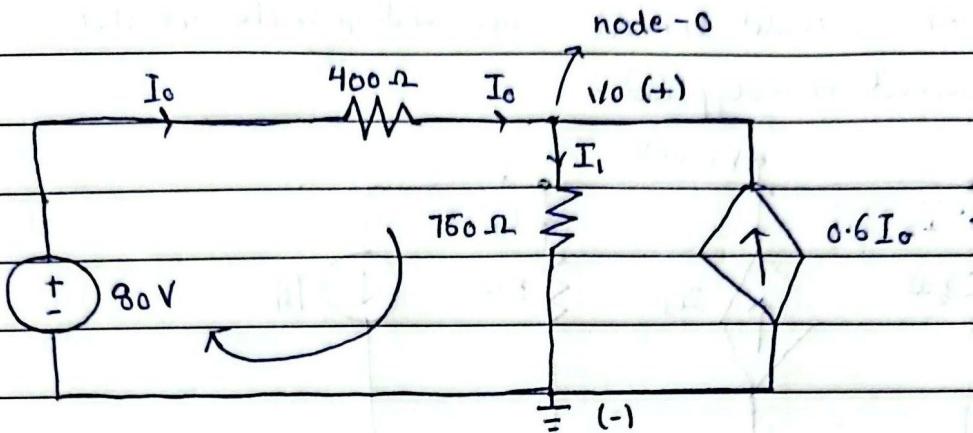

Applying KCL at the node - 0 :

$$\Rightarrow \sum I_{\text{entering}} = \sum I_{\text{leaving}}$$

$$\Rightarrow I_o + 0.6 I_o = I_i$$

$$\Rightarrow 1.6 I_o = I_i$$

Applying KVL in the loop to express I_o in terms of V_o :

$$\Rightarrow \sum V_{\text{rise}} = \sum V_{\text{drop}}$$

$$\Rightarrow 80 = I_o (400) - V_o$$

$$80 - V_o = I_o$$

$\frac{400}{}$

$$\therefore 1.6 \left(\frac{80 - V_o}{400} \right) = \frac{V_o}{750}; \quad \frac{128 - 1.6 V_o}{400} = \frac{V_o}{750}$$

$$(128 - 1.6 V_o) 750 = V_o (400)$$

$$(128 - 1.6 V_o) (1.875) = V_o$$


$$240 - 3V_o = V_o$$

$$\Rightarrow 240 = V_o + 3V_o$$

$$\Rightarrow 240 = 4V_o$$

$$\Rightarrow V_o = 60 \text{ V}$$

in a simpler way;

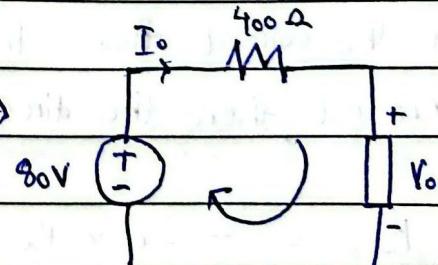


∴ Applying KVL ;

$$\Rightarrow \sum V_{\text{rise}} = \sum V_{\text{drop}}$$

$$\Rightarrow 80 = I_o (400) + 60; \quad I_o = 50 \text{ mA}$$

Q. Find i_1 & i_2

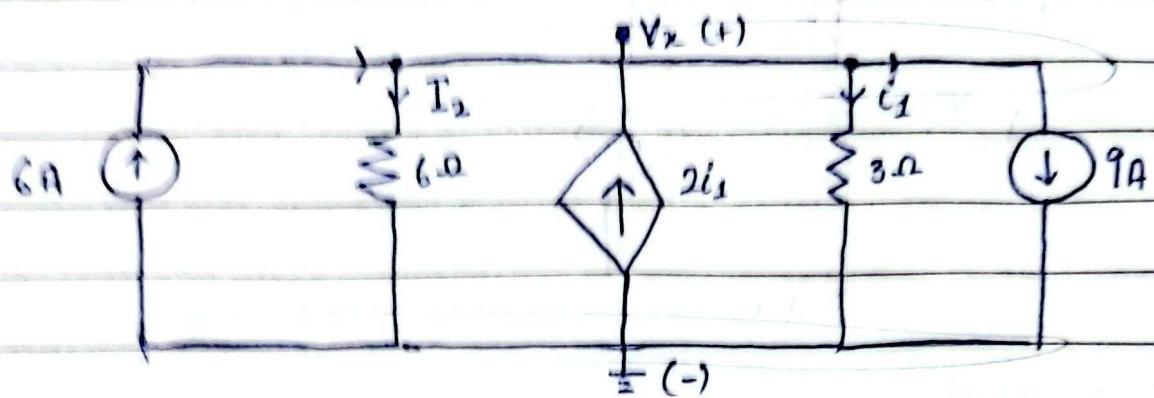Calculate power for controlled current source and indicate whether the power is absorbed or supplied.



Applying KCL at V_x :

$$\Rightarrow \sum I_{\text{ent}} = \sum I_{\text{leaving}}$$

$$\Rightarrow 6 + 2i_1 = i_2 + i_3 + 9$$

$$\therefore 6 + 2 \left[\frac{V_x}{3} \right] = \left[\frac{V_x}{6} \right] + \left[\frac{V_x}{3} \right] + 9$$

$$\Rightarrow V_x = 18V$$

$$\Rightarrow V = \underline{\underline{R}}$$

$$\Rightarrow V_x = i_3 (3\Omega)$$

$$18 = i_3 (3)$$


$$\underline{i_3 = 6A}$$

If the current flows from the negative terminal to the positive terminal, then the direction of current is opposite.

$$\begin{aligned} \Rightarrow P_{2i_1} &= -2i_1 \times V_x && 2i_1 \text{ is flowing from } -ve \text{ to} \\ &= (-2)(6)(18) && +ve \text{ terminal through current source.} \\ &= (-12)(18) = -216W \end{aligned}$$

Date: _____

Q. Find V_o :-

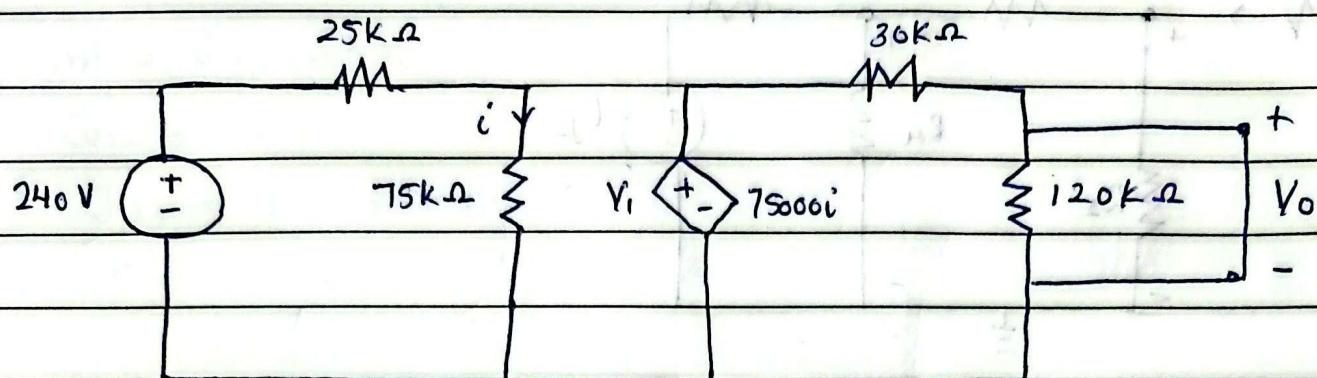


$$i_y = \frac{V_1 - V_2}{75k\Omega}$$

$$V_1 = V_2 + 75000i$$


$$i_y = \frac{V_1 - V_3}{25k\Omega} = \frac{V_2 + 75000i - V_3}{25k\Omega}$$

$$i_y = \frac{V_3 - V_4}{30k\Omega} = \frac{V_3 - V_2 - 75000i}{30k\Omega}$$
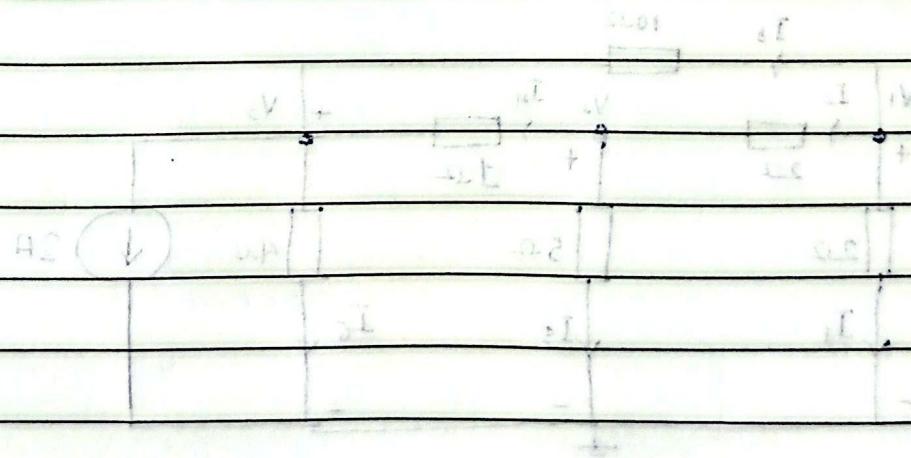
$$i_y = \frac{V_4 - V_5}{120k\Omega} = \frac{V_2 + 75000i - V_5}{120k\Omega}$$


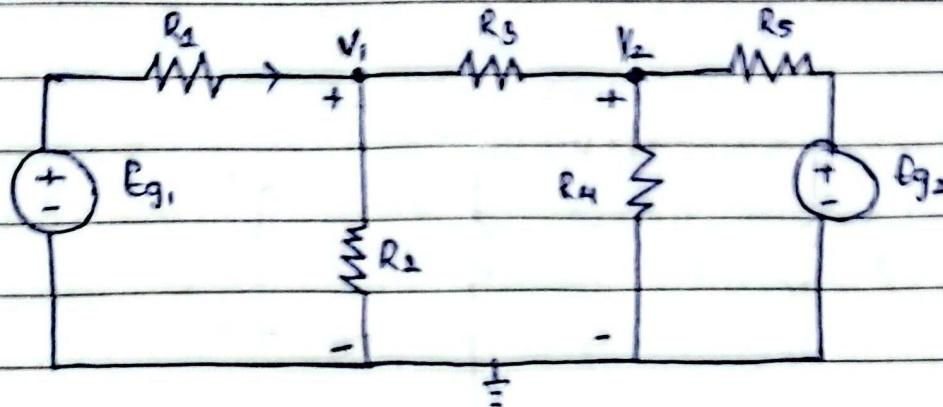
$$\therefore R_{in} = \frac{V_i}{I_i} = \frac{V_i}{A_2 V_i} = \frac{1}{A_2}$$



$$\begin{bmatrix} \bar{I}_{g_1} \\ \bar{I}_{g_2} \end{bmatrix} = \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$\bar{I}_{n \times 1} = G_{n \times n} V_{n \times 1}$$

■ $\bar{I}_{g_1} = +\frac{E_{g_1}}{R_1}, \quad \bar{I}_{g_2} = \frac{E_{g_2}}{R_5}$

$$G_{11} = G_{11} + G_{12} + G_{13}$$

$$G_{12} = G_{121} = -G_{13}$$

$$G_{13} = G_{13} + G_{14} + G_{15}$$

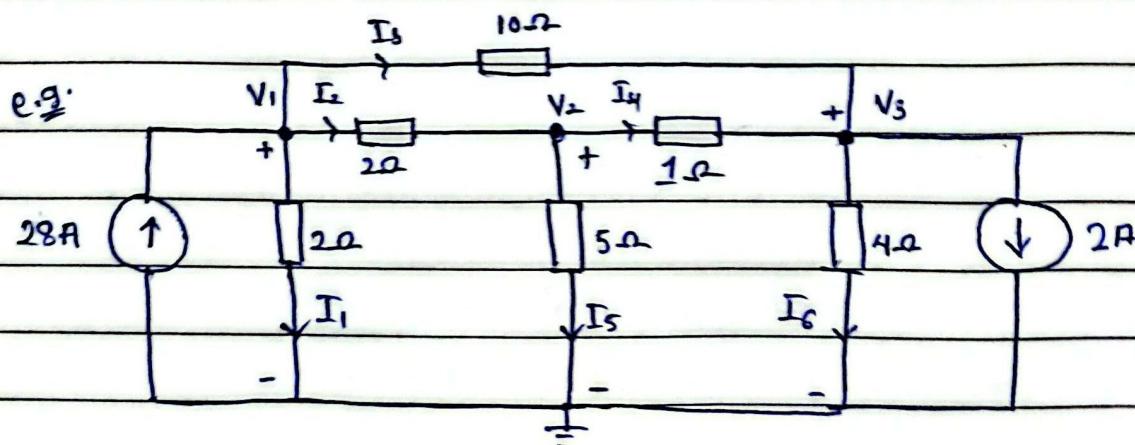

Nodal eqs :-

$$\begin{bmatrix} \bar{I}_{g_1} \\ \bar{I}_{g_2} \\ \bar{I}_{g_3} \end{bmatrix} = \begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} ; \quad \begin{aligned} \bar{I}_{g_1} &= 28A \\ \bar{I}_{g_2} &= 0A \\ \bar{I}_{g_3} &= -2A \end{aligned}$$

Date: _____

$$G_{11} = \frac{1}{2} + \frac{1}{2} + 1 = 1.125 \quad \checkmark$$

$$G_{12} = G_{21} = -\frac{1}{2} = -0.525 \quad \checkmark$$

$$G_{13} = G_{31} = -\frac{1}{10} = -0.1 \quad \checkmark$$

$$G_{22} = 1 + \frac{1}{5} + \frac{1}{2} = 1.7 \quad \checkmark$$

$$G_{23} = G_{32} = -1 \quad \checkmark$$

$$G_{33} = \frac{1}{10} + 1 + \frac{1}{4} = 1.35 \quad \checkmark$$

$$\therefore \begin{bmatrix} 28 \\ 0 \\ -2 \end{bmatrix} = \begin{bmatrix} 1.1 & -0.5 & -0.1 \\ -0.5 & 1.7 & -1 \\ -0.1 & -1 & 1.35 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$\Rightarrow 28 = 1.1v_1 - 0.5v_2 - 0.1v_3$$

$$0 = -0.5v_1 + 1.7v_2 - v_3$$


$$-2 = -0.1v_1 - v_2 + 1.35v_3$$

Cramer's rule can be applied to solve this system

of simultaneous equations ;

④ If the voltage of a node is known, then we will not apply KCL at that node.

Date: _____

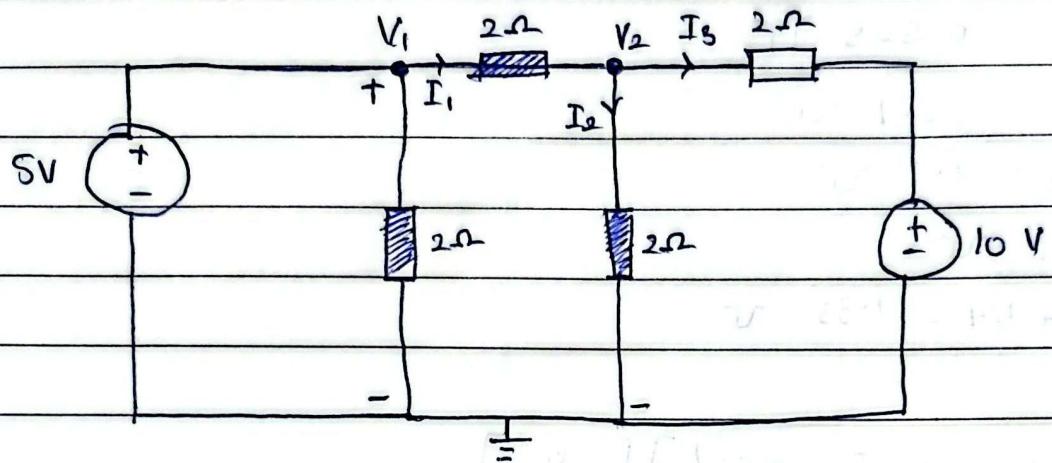

$$V_1 = 5V$$

⇒ Applying KCL at node -2 :-

$$\sum I_{\text{ent}} = \sum I_{\text{leaving}}$$

$$I_1 = I_2 + I_3 \quad | \quad 5 - V_2 = 2V_2 - 10$$


$$\frac{5 - V_2}{2} = \frac{V_2}{2} + \frac{V_2 - 10}{2} \quad | \quad -V_2 - 2V_2 = -10 - 5$$

$$(5 - V_2) = V_2 + (V_2 - 10) \quad | \quad V_2 = 5V$$

• Current flows from a higher (+) (+) voltage towards a lower (-) (-) voltage.

Date: _____

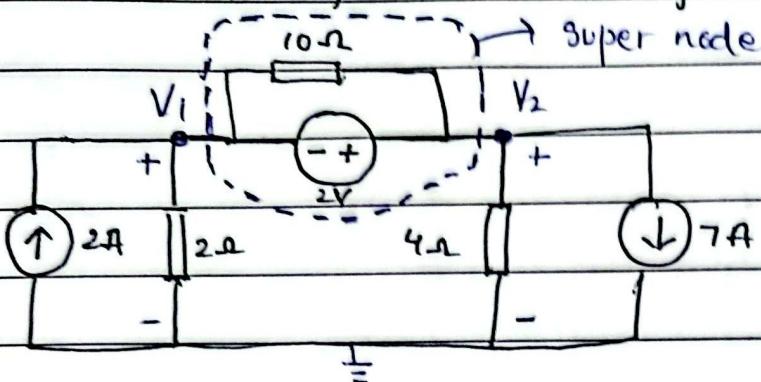Q. For the circuit, find nodal voltages :-



Applying KCL on the super node :

$$\Rightarrow \sum I_{\text{entering}} = \sum I_{\text{leaving}}$$

$$\Rightarrow 2 = i_{2,2} + i_{4,2} + 7$$

$$\Rightarrow 2 - 7 = \frac{V_1}{2} + \frac{V_2}{4} - ①$$

⇒ Applying KVL on the super node ;

$$\Rightarrow \sum V_r = \sum V_d$$


Solving the two eq. simultaneously ;

$$\Rightarrow V_1 + 2 = V_2 - ②$$

$$\therefore V_1 = -7.33 \text{ V}$$

$$V_2 = -5.33 \text{ V}$$

Q. for the circuit, find i :-

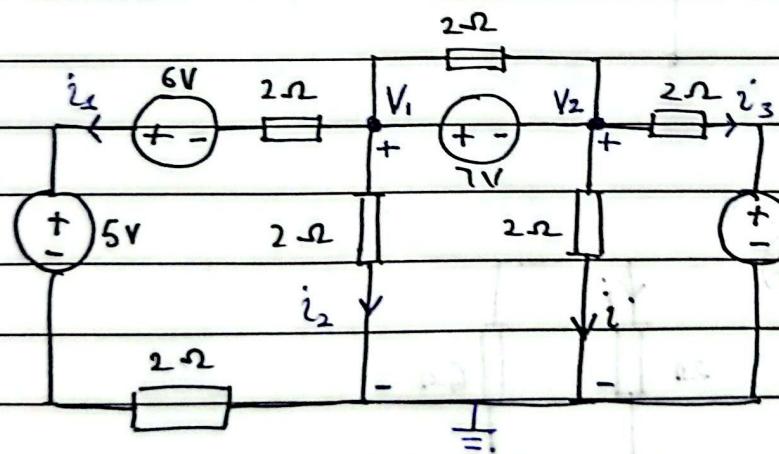

Applying KCL on the super node ;

$$\Rightarrow \sum I_{\text{ent}} = \sum I_{\text{leav}}$$

$$\Rightarrow 0 = i_1 + i_2 + i + i_3$$

$$\Rightarrow 0 = \left(\frac{V_1 - 5 + 6}{4} \right) + \left(\frac{V_1}{2} \right) + \left(\frac{V_2}{2} \right) + \left(\frac{V_2 - 9}{2} \right)$$

$$\Rightarrow 0 = V_1 - 5 + 6 + 2V_2 + 2V_2 + 2V_2 - 16$$

$$0 = V_1 + 1 + 2V_1 + 2V_2 + 2V_2 - 16$$

$$0 = 3V_1 + 4V_2 - 15$$

$$-3V_1 = 4V_2 - 15 ; V_1 = \frac{4V_2 - 15}{3} ; V_1 = \frac{15 - 4V_2}{3}$$





Date: _____

$$V_1 = V_2 + 7 = (2)$$

$$V_1 = \frac{15 - V_2}{3} = (1)$$

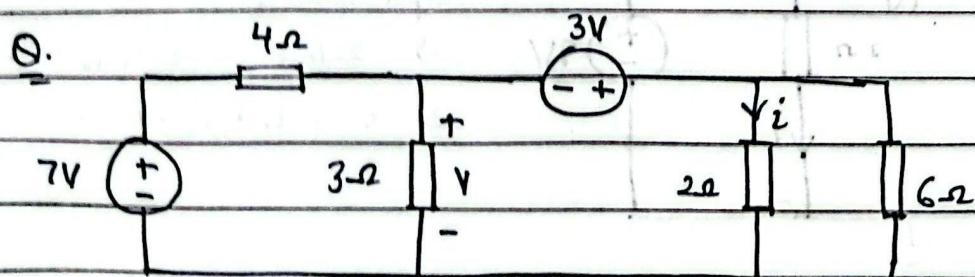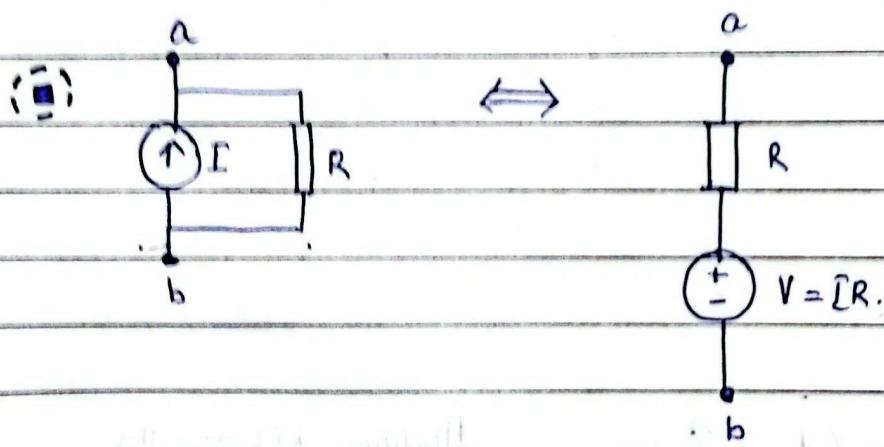\Rightarrow Solving the two eq. simultaneously:




Apply mesh analysis :-

$$\begin{bmatrix} 7 \\ 3 \\ 0 \end{bmatrix} = \begin{bmatrix} 7 & -3 & 0 \\ -3 & 5 & -2 \\ 0 & -2 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Total resistance of the different loops

Date: _____

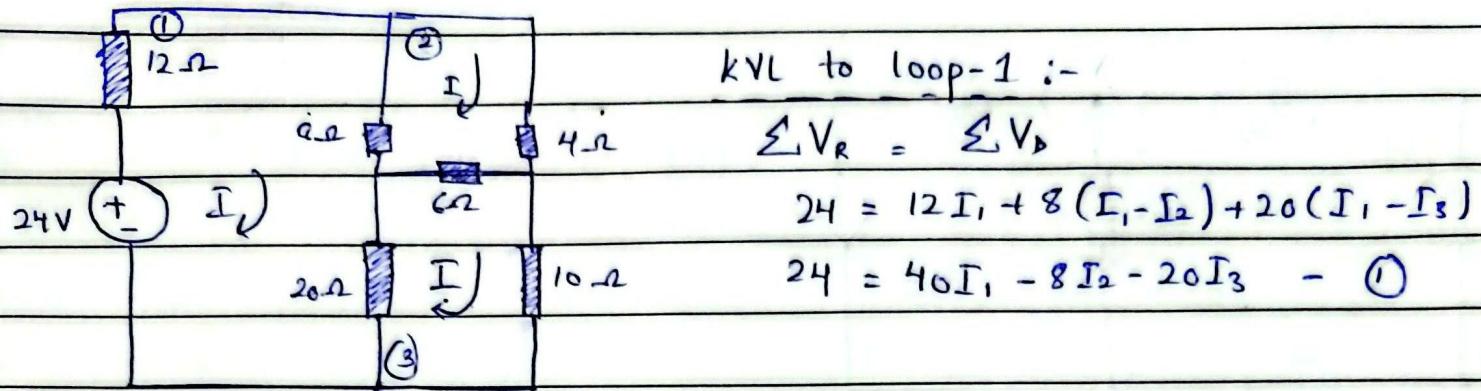Q. Use mesh analysis to find the voltage across the 6Ω resistor :-



KVL to loop-1 :-

$$\sum V_R = \sum V_D$$

$$24 = 12I_1 + 8(I_1 - I_2) + 20(I_1 - I_3) \quad \text{--- (1)}$$

$$24 = 40I_1 - 8I_2 - 20I_3 \quad \text{--- (1)}$$

KVL to loop-2 :-

$$\sum V_R = \sum V_D$$

$$0 = 8(I_2 - I_1) + 6(I_2 - I_3) + 4I_2$$

$$0 = -8I_1 + 18I_2 - 6I_3 \quad \text{--- (2)}$$

KVL to loop-3 :-

$$\sum V_R = \sum V_D$$

$$0 = 20(I_3 - I_1) + 6(I_3 - I_2) + 10I_3$$

$$0 = -20I_1 + 20I_3 + 6I_3 - 6I_2 + 10I_3$$

$$0 = -20I_1 + 20I_3 + 6I_3 + 10I_3 - 6I_2$$


$$0 = -20I_1 + 36I_3 - 6I_2 \quad \text{--- (3)}$$

Solving all the three equations simultaneously ;

$$\Rightarrow I_1 = 1.125 \text{ A}$$

$$I_2 = I_3 = 0.75 \text{ A}$$

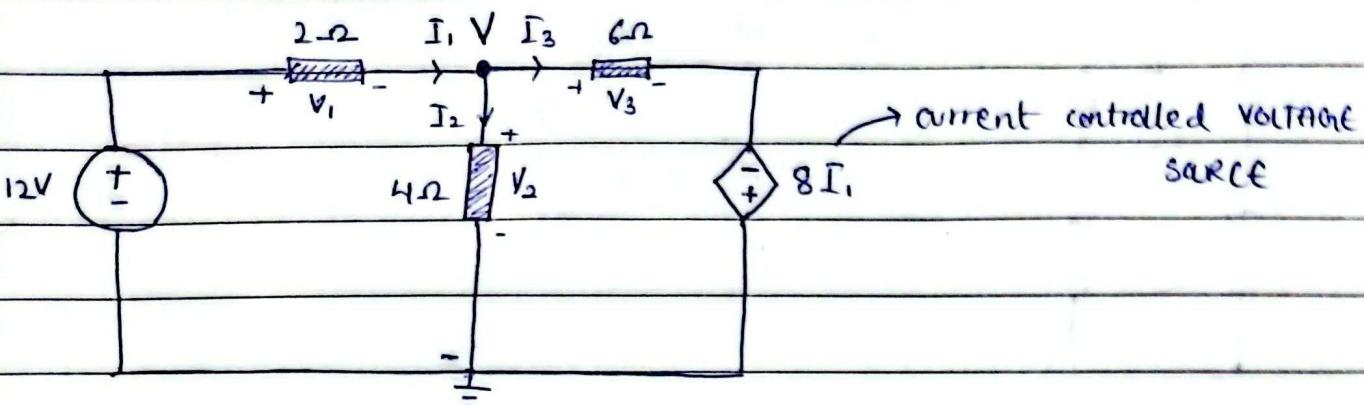Q2. Calculate the unknown currents and voltages in the following circuit :-



Applying nodal analysis :-

$$\sum I_{\text{ent}} = \sum I_{\text{leav}}$$


$$I_1 = I_2 + I_3$$

$$\frac{12-V}{2} = \frac{V}{4} + \left(\frac{V + 8I_1}{6} \right)$$

$$\Rightarrow \frac{12-V}{2} = \frac{V}{4} + \left(V + \left(\frac{12-V}{2} \right) \right)$$

Date: _____

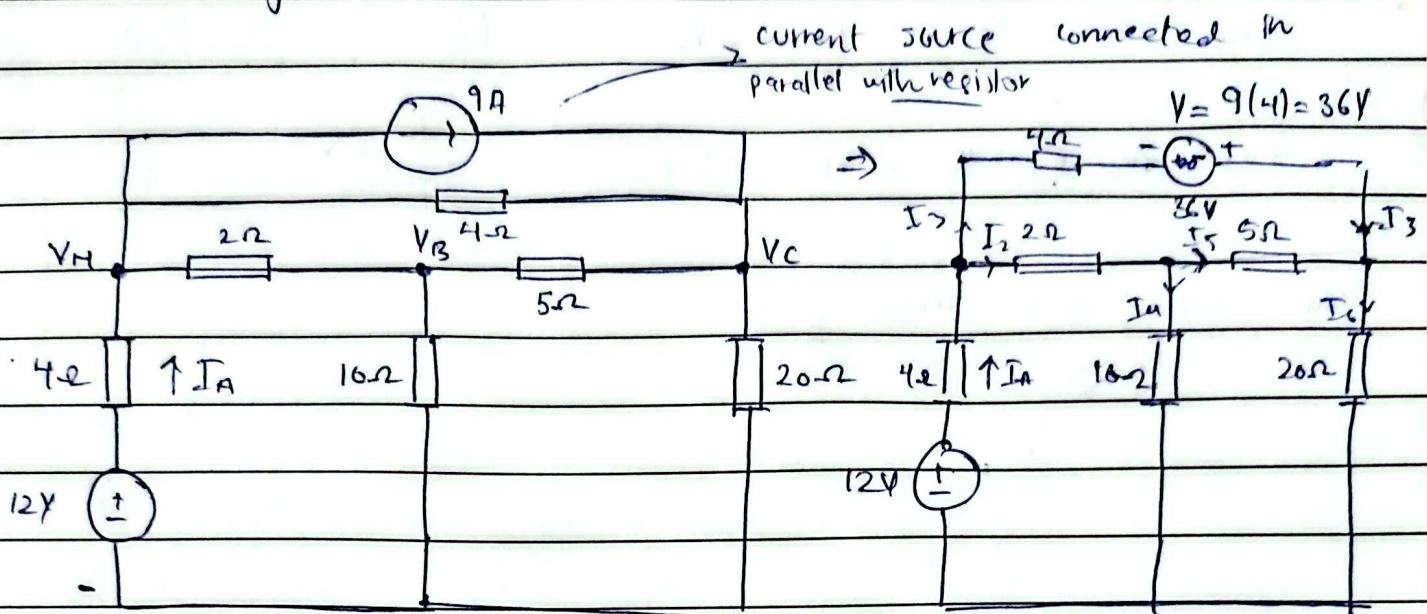Expt. find the voltage across 5Ω resistor and the current I_A through the $12V$ source.



KCL at node - 0 :-

$$\sum I_{\text{ent}} = \sum I_{\text{exit}}$$

$$\Rightarrow I_A = I_2 + I_3$$

$$\Rightarrow \frac{12 - V_A}{4} = \left(\frac{V_A - V_B}{2 \times 2} \right) + \left(\frac{V_A + 36 - V_C}{4} \right); 12 - V_A = 2V_A - 2V_B + V_A + 36 - V_C$$

KCL at node - 1 :-

$$\sum I_{\text{ent}} = \sum I_{\text{exit}}$$

$$\Rightarrow I_2 = I_4 - I_5$$

$$\Rightarrow \frac{V_A - V_B}{2 \times 5} = \frac{V_B + 1}{10 \times 1} + \left(\frac{V_B - V_C}{5 \times 2} \right); 5V_A - 5V_B = V_B + 2V_B - 2V_C$$

$$\Rightarrow 5V_A - 5V_B = V_B + 2V_B - 2V_C$$

KCL at node - 2 :-

$$\Rightarrow \sum I_{\text{ent}} = \sum I_{\text{exit}}$$

$$\Rightarrow I_4 = I_5 + I_3 = I_C$$

$$\Rightarrow \left(\frac{V_B - V_C}{5 \times 4} \right) + \left(\frac{V_A + 36 - V_C}{4 \times 5} \right) = V_C; 4V_B - 4V_C + 5V_A + 180 - 5V_C = V_C$$

Date: _____

$$12 - V_A = 2V_A - 2V_B + V_A + 36 - V_C \quad - \textcircled{1}$$


$$5V_A - 5V_B = V_B + 2V_B - 2V_C \quad - \textcircled{2}$$

$$4V_B - 4V_C + 5V_A + 180 - 5V_C = V_C \quad - \textcircled{3}$$

Simultaneously solve these eq. :-

If a current-controlled voltage source was connected, instead of the current source, then, $V_2 = 4I_1$; since there is no resistor
 = Connected. Date: _____

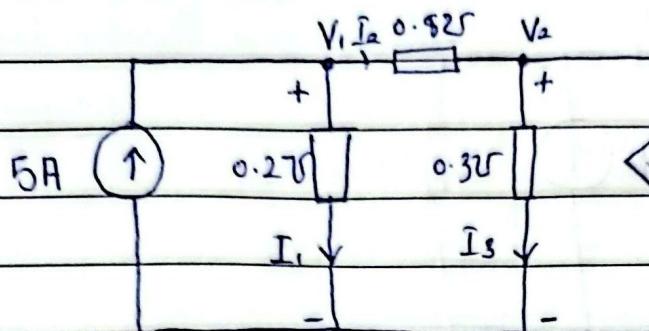Q. Find the voltage across $0.8\text{ }G$ conductance :-



KCL at j-1 :-

$$\Rightarrow \sum I_{ent} = \sum I_{ex}$$

$$\Rightarrow S = I_1 + I_2$$

KCL at j-2 :-

$$\Rightarrow \sum I_{ent} = \sum I_{ex}$$

$$\Rightarrow I_2 = I_3 + 4I_1$$

Since conductances are given, in calculations involving $V = IR$, the inverse will be taken.

\Rightarrow KCL at j-1 :-

$$\Rightarrow 5 = 0.2V_1 + 0.8(V_1 - V_2)$$

$$\Rightarrow S = V_1 - 0.8V_2$$

\Rightarrow KCL at j-2 :-

$$\Rightarrow I_2 = I_3 + 4I_1$$

$$\Rightarrow 0.8(V_1 - V_2) = 0.3V_2 + 4(0.2V_1)$$

$$\Rightarrow 0.8V_1 - 0.8V_2 = 0.3V_2 + 0.8V_1$$

$$\Rightarrow -0.8V_2 - 0.3V_2 = 0$$

$$\Rightarrow \therefore V_2 = 0$$



\therefore Voltage ACROSS $0.8\text{ }G$ conductance

$$\Rightarrow V_{0.82G} = S - 0 = 5\text{ V.}$$

$$\therefore S = V_1 - 0.8(0)$$


$$\Rightarrow V_1 = 5$$

Q. Calculate V_B and I_3 :-

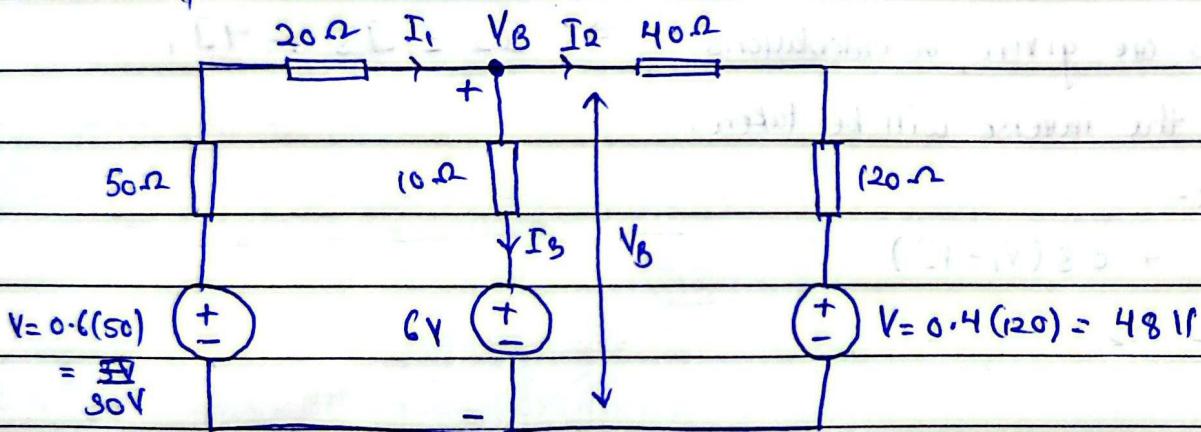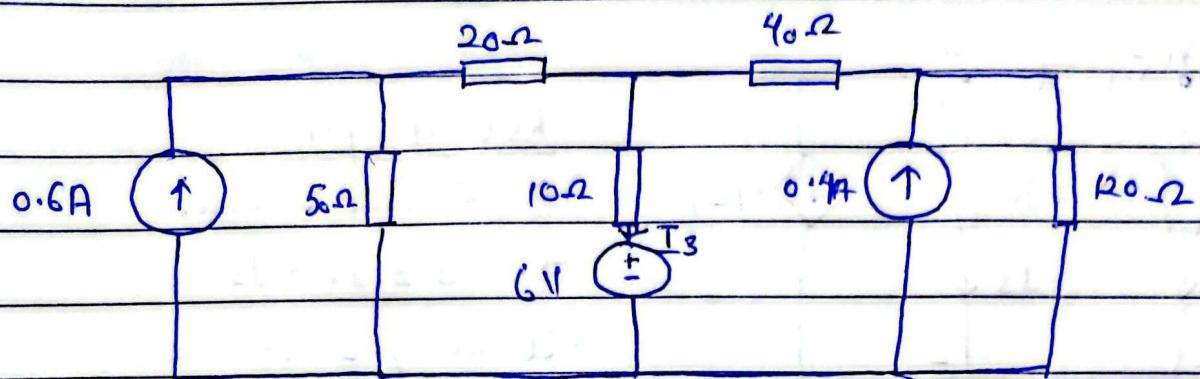

⇒

Q. Using nodal analysis, find V :-

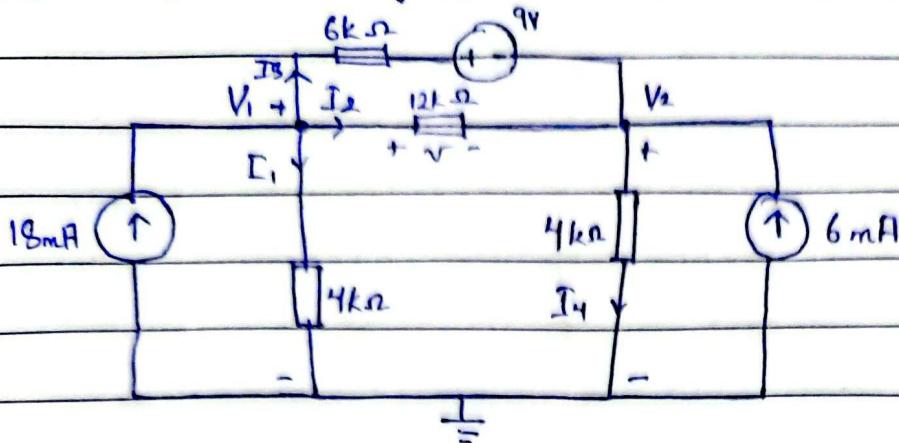

KCL at $j=1$:-

$$\Rightarrow 18m = I_1 + I_2 + I_3$$

$$18m = \frac{V_1}{4k} + \frac{V_1 - V_2}{12k} + \frac{V_1 - 9 - V_2}{6k}$$

$$\frac{18m + 9}{6k} = \left[\frac{1}{4k} + \frac{1}{12k} + \frac{1}{6k} \right] V_1 + \left[-\frac{1}{6k} - \frac{1}{12k} \right] V_2 \quad - \textcircled{1}$$

KCL at $j=2$:-

$$I_3 + I_2 + 6m = I_4$$


$$\left(\frac{V_1 - 9 - V_2}{6k} \right) + \left(\frac{V_1 - V_2}{12k} \right) + 6m = \frac{V_2}{4k}$$

$$\frac{6m - 9}{6k} = \left[-\frac{1}{6k} - \frac{1}{12k} \right] V_1 + \left[\frac{1}{6k} + \frac{1}{12k} + \frac{1}{4k} \right] V_2 \quad - \textcircled{2}$$


$$\Rightarrow I = G \nabla V$$

$$\begin{bmatrix} 18m + \frac{9}{6k} \\ 6m - \frac{9}{6k} \end{bmatrix} = \begin{bmatrix} \frac{1}{6k} + \frac{1}{12k} + \frac{1}{4k} & -\frac{1}{12k} - \frac{1}{6k} \\ -\frac{1}{12k} - \frac{1}{6k} & \frac{1}{4k} + \frac{1}{12k} + \frac{1}{6k} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Q. Use mesh analysis for loop currents.

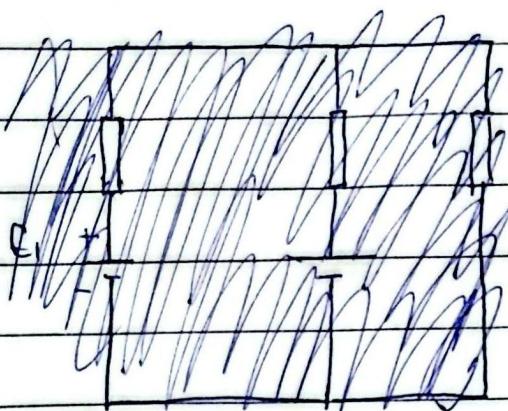

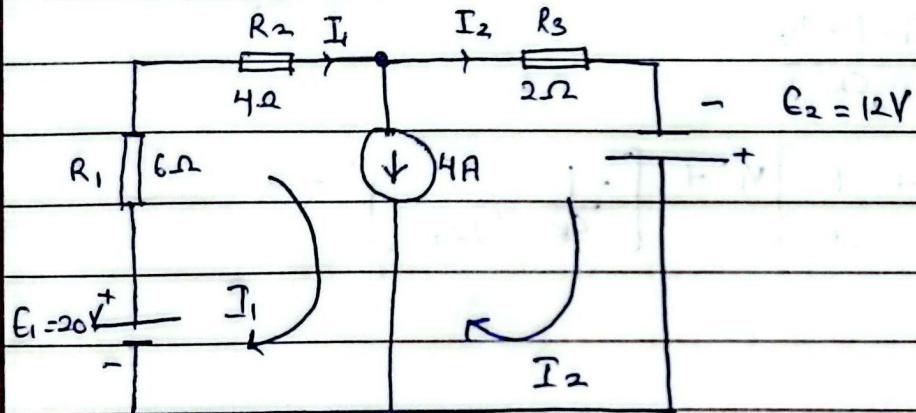SUPER MESH : \rightarrow KCL + KVL is applied on a super mesh (only once)



- Identify the loops, assign loop currents in CW direction, remove the current source and apply KVL to resulting loops.
↳ Apply KVL collectively on all the loops.

KVL

$$\sum V_r = \sum V_d$$

$$\Rightarrow 20 + 12 = 6I_1 + 4I_1 + 2I_2$$

$$32 = 10I_1 + 2I_2 \quad \text{--- (1)}$$


KCL

$$\sum I_{ext} = \sum I_{leaf}$$

$$\Rightarrow I_1 = 4 + I_2 \quad \text{--- (2)}$$

Date: _____

Q. Find the loop currents :-

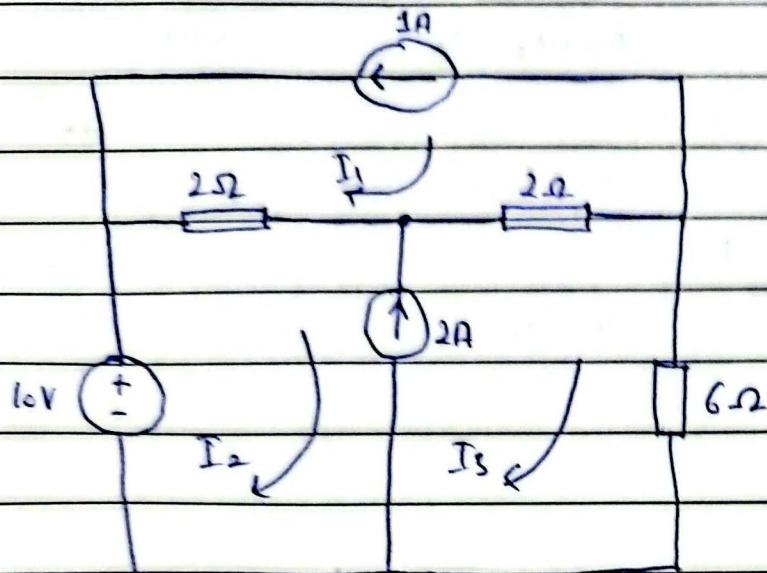

Applying KVL on the supermesh :-

$$\Rightarrow \sum V_r = \Delta V_d$$

$$\Rightarrow 10 = 2(I_2 - I_1) + 2(I_3 - I_1) + 6I_3$$

$$10 = 2I_2 - 2I_1 + 2I_3 - 2I_1 + 6I_3$$

$$10 = -4I_1 + 2I_2 + 8I_3$$

$$10 = 2(-2I_1 + I_2 + 4I_3)$$

$$5 = -2I_1 + I_2 + 4I_3$$

$$\Rightarrow 5 = -2I_1 + I_2 + 4I_3 \quad \text{--- (1)}$$

$$\Rightarrow I_1 = -1 \quad \text{--- (2)}$$


Applying KCL on the supermesh :-

$$\Rightarrow \sum I_{\text{ent}} = \sum I_{\text{exit}}$$

$$\Rightarrow I_2 + 2 = I_3 \quad \text{--- (3)}$$

TRANSFORMATIONS


Date: _____

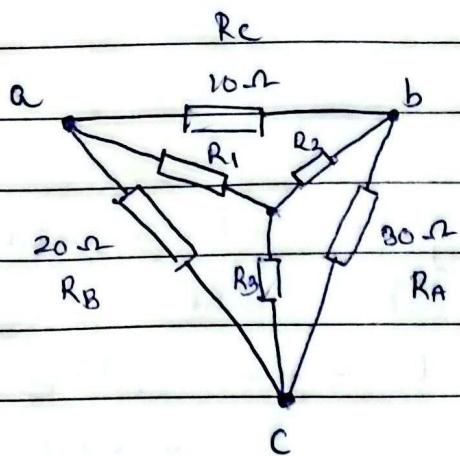

$$\Rightarrow R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(20)(10)}{30 + 20 + 10} = 3.33 \Omega$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(30)(10)}{30 + 20 + 10} = 5 \Omega$$
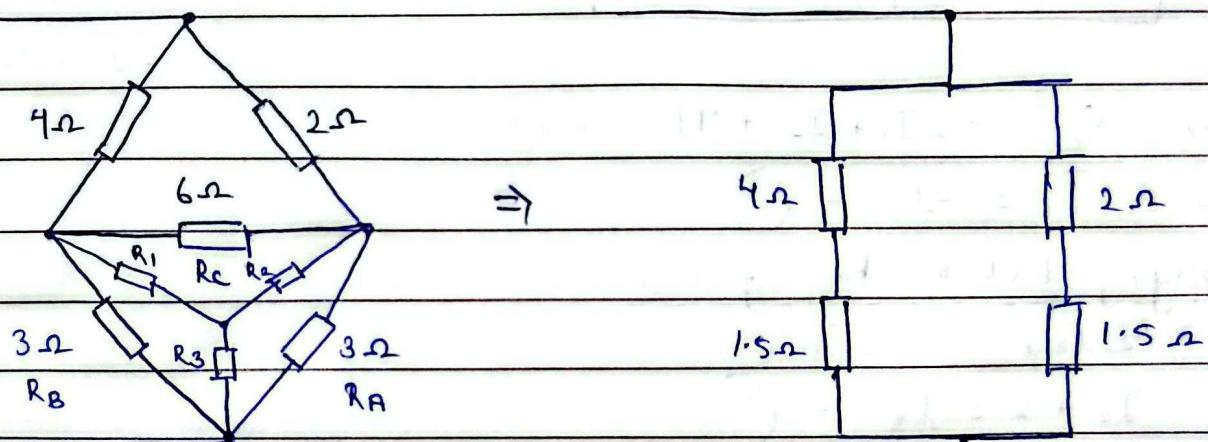
$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(30)(20)}{30 + 20 + 10} = 10 \Omega$$



$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(3)(6)}{3 + 3 + 6} = 1.5 \Omega$$


$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(3)(6)}{3 + 3 + 6} = 1.5 \Omega$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(3)(3)}{3 + 3 + 6} = 0.75 \Omega$$

$$R_T = [5.5 || 3.5] + 0.75$$

- If all the resistances in a Δ -form are the same, then the equivalent resistance in the Y -form are all the same; $\Rightarrow R_1 = R_2 = R_3 = \frac{R^2}{3R} = \frac{R}{3}$; R = resistance Date:

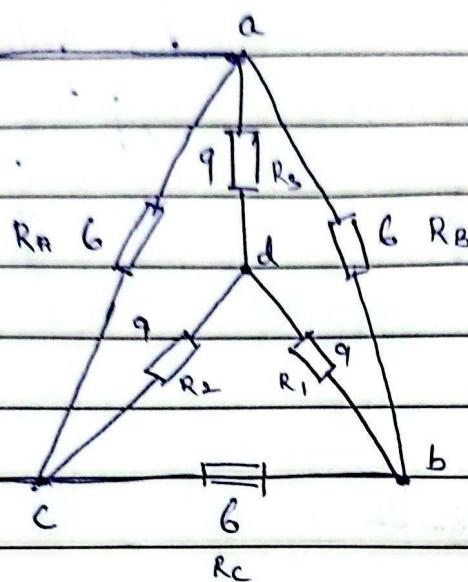Find the equivalent resistance, $R_T = ?$




Transforming the outer;

$$\Delta \rightarrow Y :$$

$$\Rightarrow R_1 = R_B R_C = R = \frac{6}{3} = 2 \text{ ohms}$$

$$\therefore R_1 = R_2 = R_3 = 2 \text{ ohms}$$

\Rightarrow


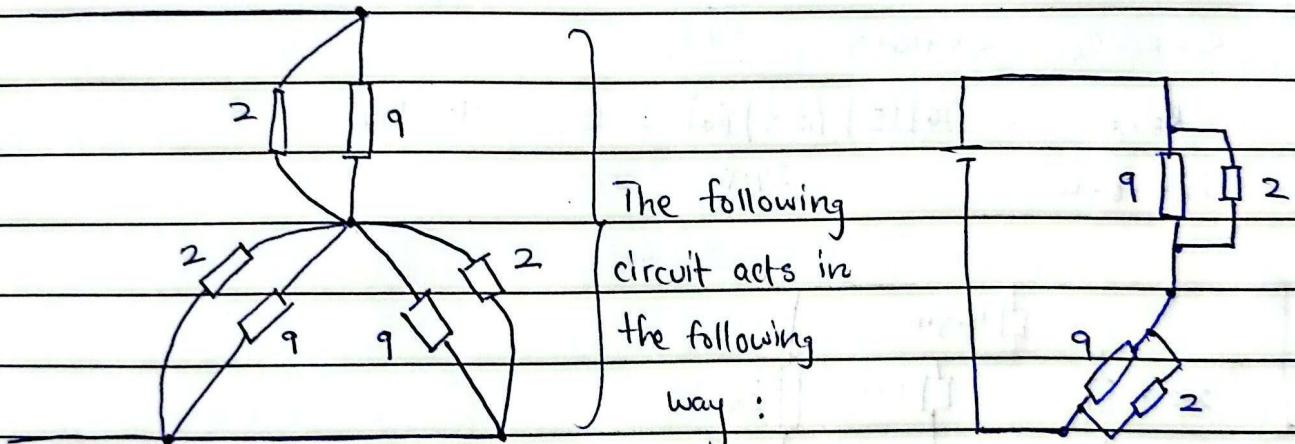


$$\Rightarrow R_T = \frac{(9)(2)}{11} + \frac{(9)(2)}{11} = \frac{1 \cdot 63}{11} + \frac{1 \cdot 63}{11} = 3.27 \text{ ohms}$$

Date:

Q. Find $R_{ab} = ?$


$$i = ?$$

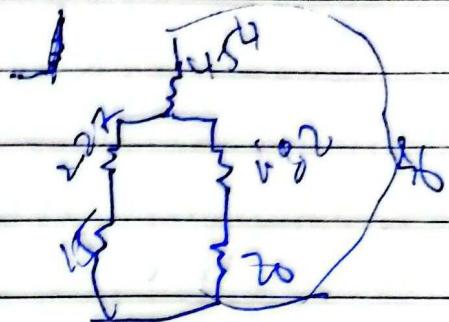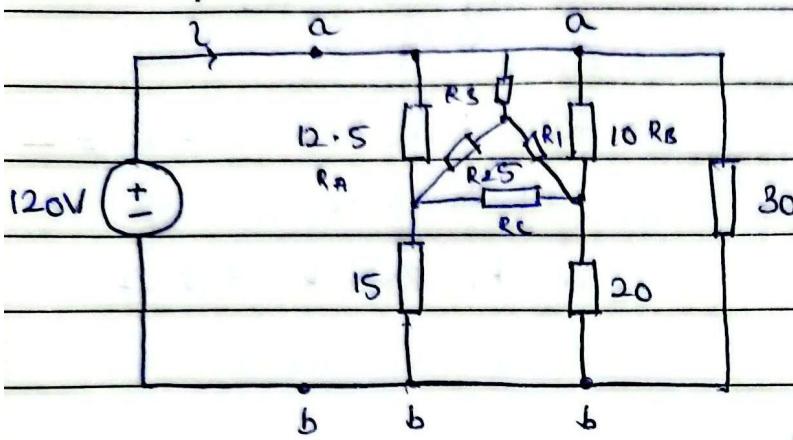

$$R_1 = R_B R_C = (10)(5) = \frac{50}{27.5} = 1.82 \Omega$$

$$R_2 = R_A R_C = (12.5)(5) = \frac{62.5}{27.5} = 2.27 \Omega$$

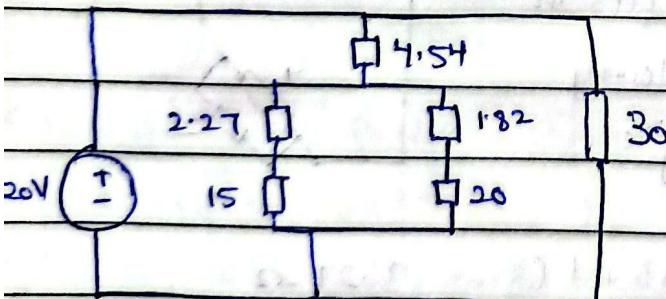
$$R_3 = R_B R_A = \frac{(10)(12.5)}{27.5} = \frac{125}{27.5} = 4.54 \Omega$$




* The dependent source SHOULD NOT be charged, when applying the superposition principle (SPT).

Date: _____

Q. Use SPT to find V_x :-

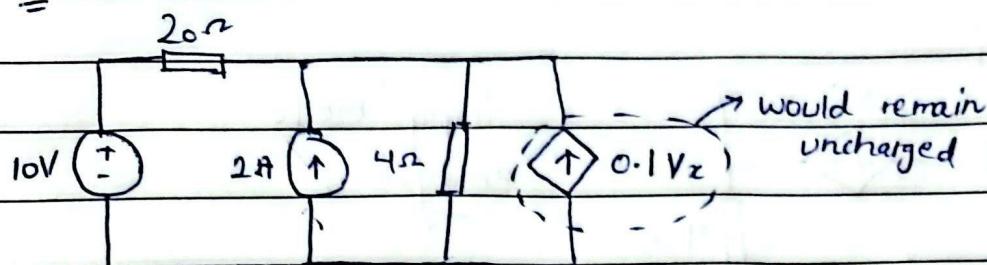


⇒ ① let us consider 10V source alone :

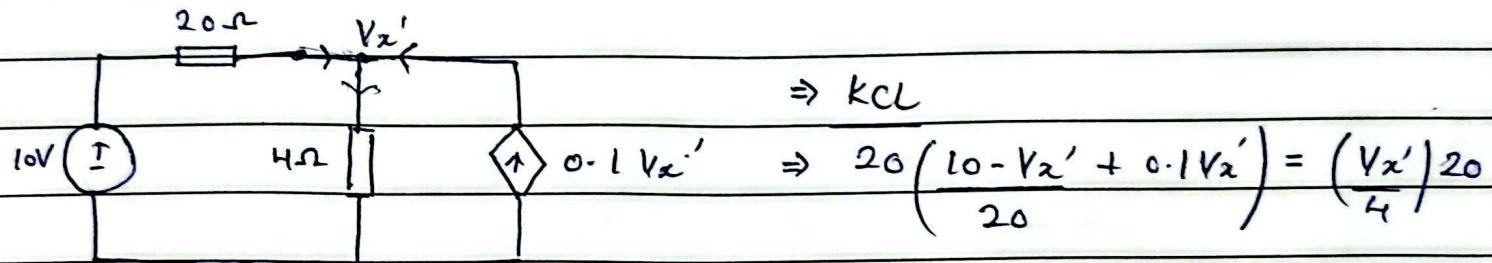

$$\Rightarrow 10 - Vx' + 2Vx' = 5Vx'$$

$$Vx' = \frac{10}{4} = 2.5V$$

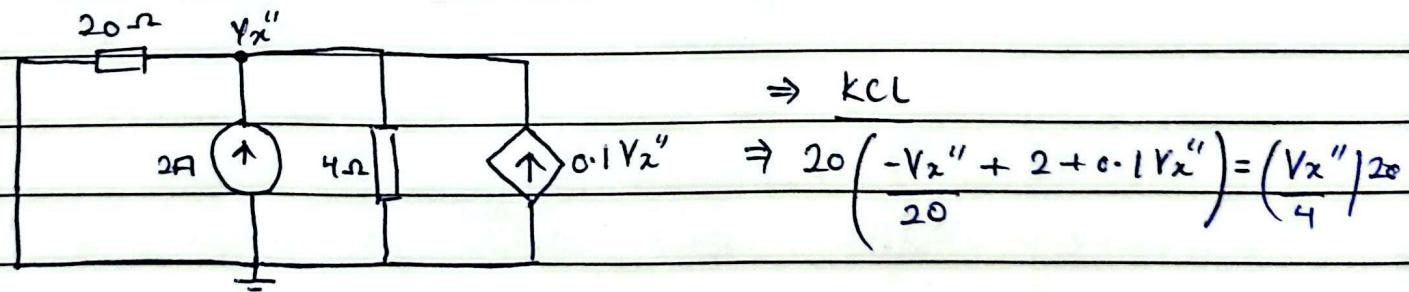⇒ ② let us consider only 2A current source in the circuit :



$$\Rightarrow Vx'' + 40 + 2Vx'' = 5Vx''$$

$$4Vx'' = 40$$

$$Vx'' = 10V$$


⇒ ③ Applying SPT :

$$\underline{\underline{Vx = Vx' + Vx'' = 12.5V}}$$

- The Superposition principle (SPT) is applied to find the dependent voltage or current source.

Date: _____

Q. Apply SPT to find $i_o = ?$

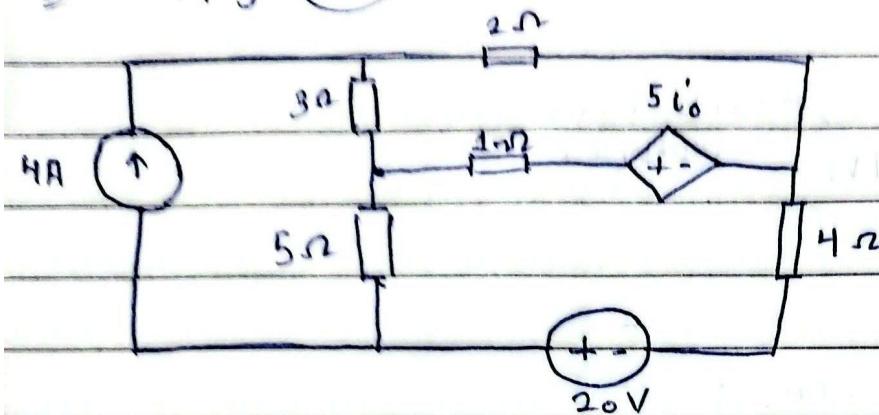

Apply mesh analysis;

$$24V = 12V + 8I - 6I$$


$$12V = 8I$$

\therefore finding $2I = 12V$ found $I = 3A$ plus 3 times $2I = 6A$

- The Superposition principle (SPT) is applied to find the dependent voltage or current source.

Date: _____

Q. Apply SPT to find $i_o = ?$

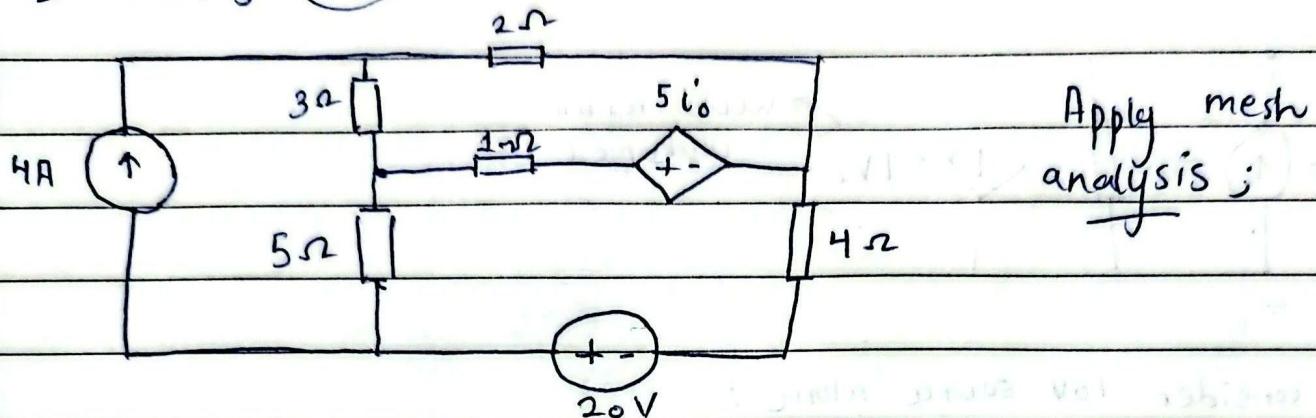

$$V_{AB} = V_{AC} + V_{CB} - 0V$$

$$V_{CB} = 0V - 20V$$

∴ $V_{AB} = V_{AC} + 20V - 0V$

$$-20V = -2V + 20V - 0V$$


$$-20V = -2V + 20V - 0V$$

$$-20V = -2V + 20V$$


Can be used to calculate the voltage and the current across a load resistor.

Thevenin's Theorem

Date: _____

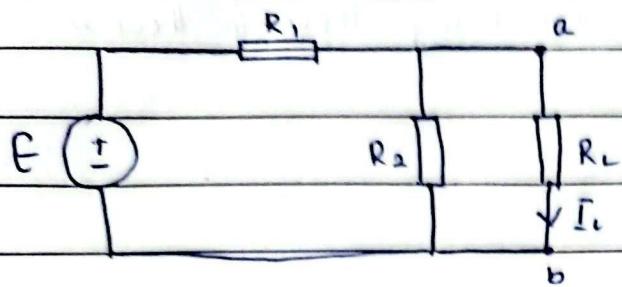


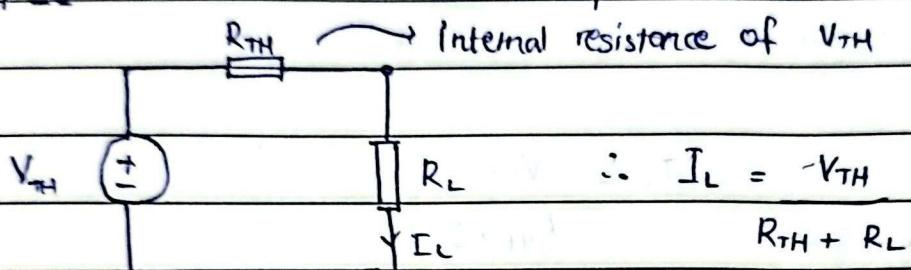Step-1 :- Draw the Thevenin equivalent circuit :-




⇒ The Thevenin equivalent circuit is a series circuit with these resistors.

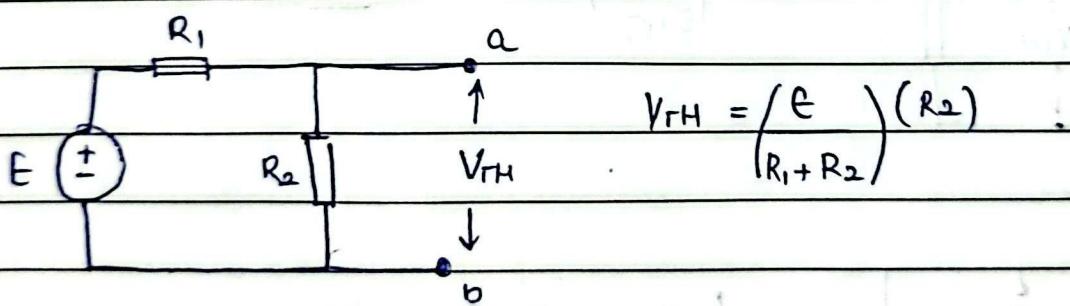
Step-2 :- Open the circuit ; the terminals **(a)** and **(b)** in the original circuit are opened. V_{TH} is the voltage that would appear across **(a)** and **(b)**.



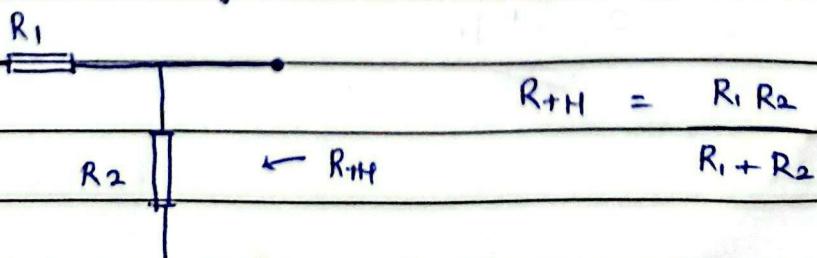
Step-3 :- Replace any independent source in the original circuits by its internal resistance. R_{TH} is the equivalent R while looking back through **(a)** and **(b)**.



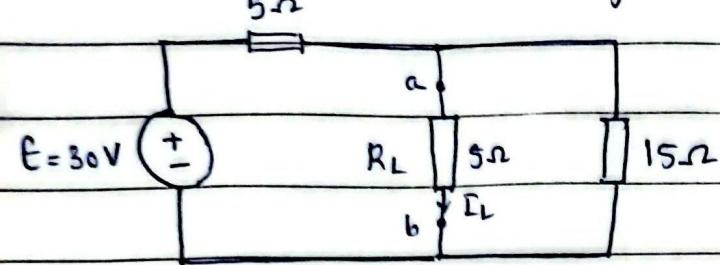
Q. find the current through 5Ω resistor using Thevenin theorem :-



⇒ The Thevenin equivalent circuit :-

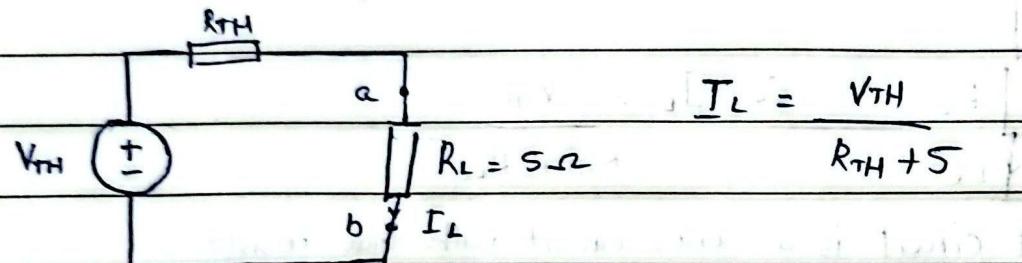


⇒

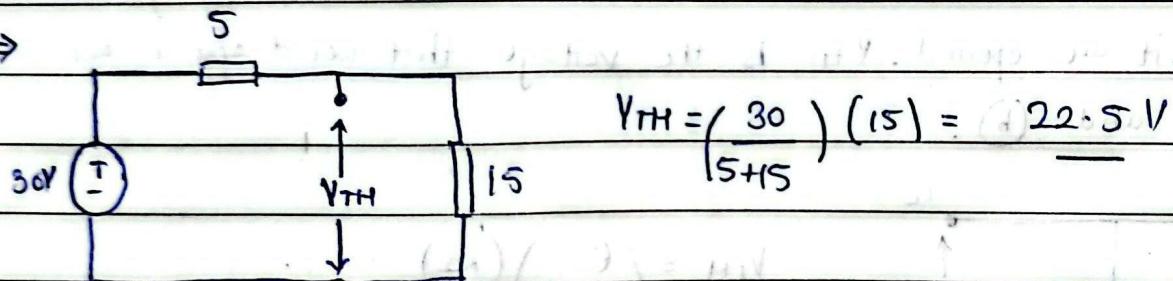

$$V_{TH} = \frac{30}{5+15} (15) = 22.5 \text{ V}$$


⇒

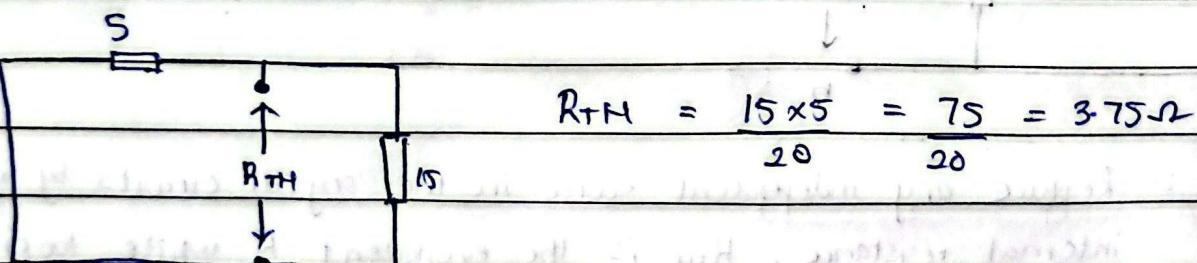

$$R_{TH} = \frac{15 \times 5}{20} = \frac{75}{20} = 3.75 \Omega$$

$$\Rightarrow \therefore I_L = \frac{22.5}{3.75 + 5} = 2.57 \text{ A}$$

Date: _____

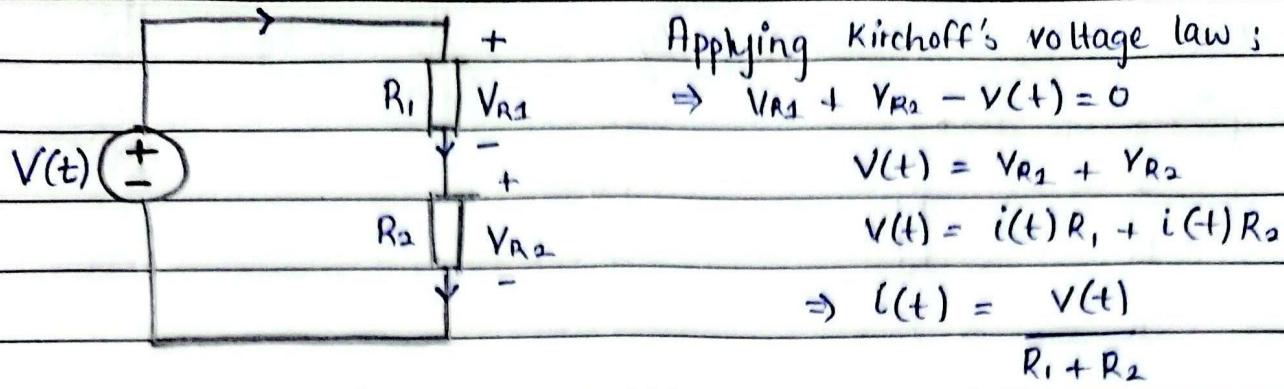


$$\therefore V_{R1} = \left(\frac{V(t)}{R_1 + R_2} \right) R_1$$

$$V_{R2} = \left(\frac{V(t)}{R_1 + R_2} \right) R_2$$

} Voltage
dividers

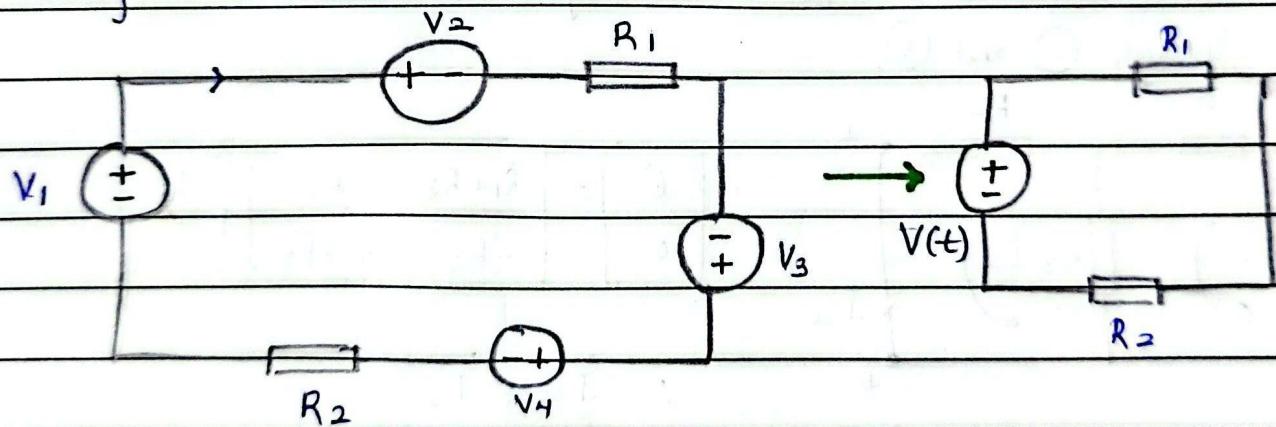
- Voltage sources can also be combined, to form a singular voltage source, using KVL :




Norton's Theorem

Date: _____

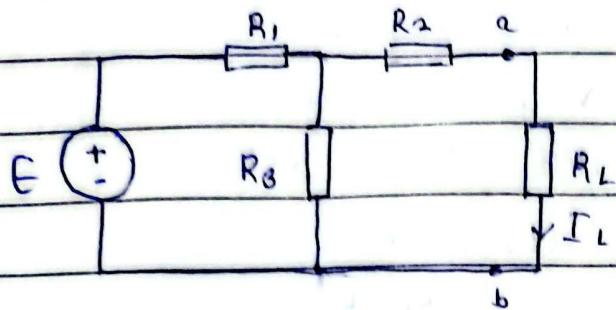
↳ applies to linear bilateral circuits only



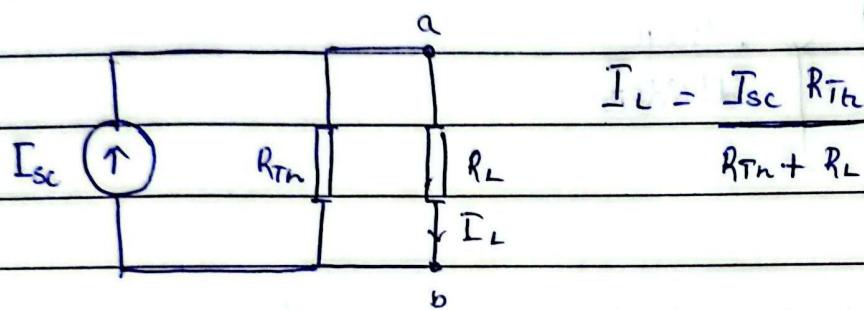
Step-1 :- Draw the Norton equivalent circuit.



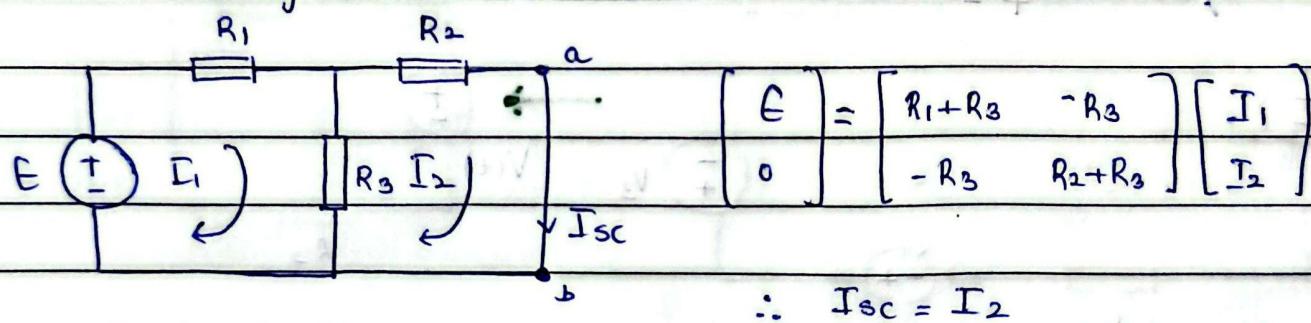Step-2 :- Short circuit \textcircled{a} and \textcircled{b} in the original circuit. I_{sc} is the current through \textcircled{a} and \textcircled{b} .




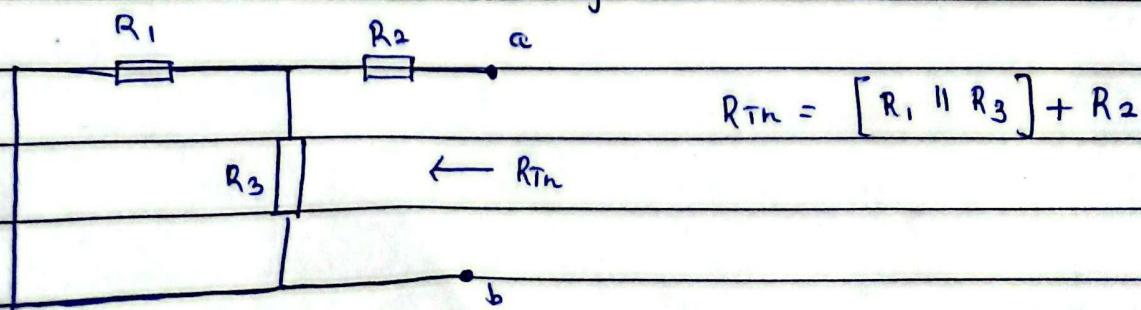Step-3 :- Open circuit \textcircled{a} and \textcircled{b} in the original circuit, and replace all independent sources by the internal resistances. R_{Tn} is the equivalent R when we look through \textcircled{a} and \textcircled{b} .



Q. In a circuit where a path of a current is short circuited, then the parallel circuit paths are ignored.

Date: _____

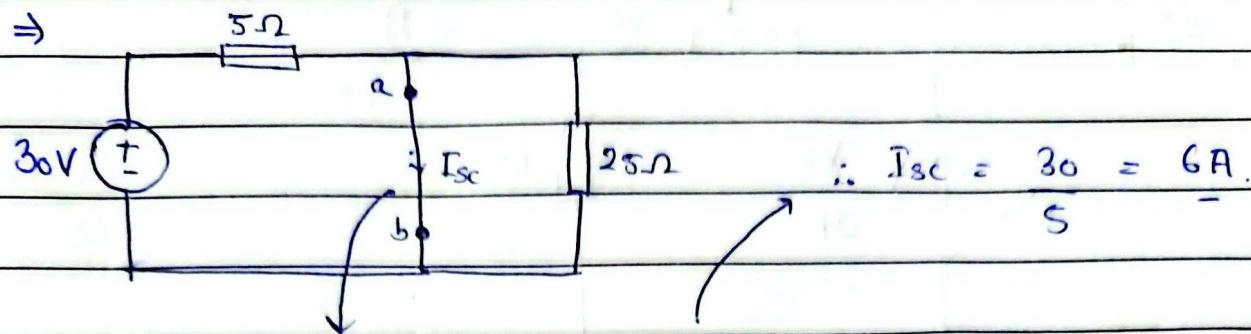

This path short circuits, rendering
the 25Ω resistor useless.

(4-12)

Q.

MAXIMUM POWER TRANSFER THEOREM :-

Example : find the condition for max power transferred to the load resistor. Also calculate the max power transferred.


Circuit Analysis

■ Current flows from high potential to low potential.

⇒ The ground node is at a lower potential, and therefore, the direction of current should be taken accordingly.

$$V = IR ; \frac{V}{R} = I$$

Q. Find the value of V_0 :-

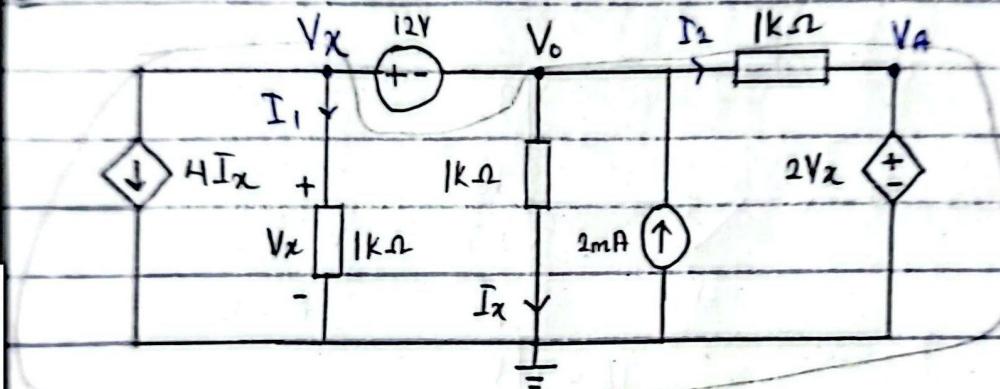

Since there is a voltage source connected between two essential nodes, node-X and node-0;

$$\Rightarrow V_x - V_0 = 12 - \textcircled{1}$$

Applying KCL at node-A :-

→ CANNOT apply, since the nodal voltage is known.

$$\Rightarrow V_A - 0 = 2V_x$$

$$V_A = 2V_x - \textcircled{2}$$

Applying KCL at the supernode :-

$$\Rightarrow \sum I_{ent} = \sum I_{leav}$$

$$\Rightarrow 2m = 4I_x + I_1 + I_x + I_2$$

$$2m = 4\left(\frac{V_0}{1k}\right) + \left(\frac{V_x}{1k}\right) + \left(\frac{V_0}{1k}\right) + \left(\frac{V_0 - V_A}{1k}\right)$$

$$2 = 4V_0 + V_x + V_0 + V_0 - V_A$$

$$2 = 6V_0 + V_x - (2V_x)$$

$$\Rightarrow 2 = 6V_0 + V_x - 2V_x$$

$$2 = 6V_0 - V_x$$

$$\Rightarrow 6V_0 - V_x = 2$$

$$\Rightarrow -V_x + 6V_0 = 2$$


$$+ V_x - V_0 = 12$$

$$5V_0 = 14$$

$$V_0 = 2.8V$$

$$\Rightarrow \underline{V_o} = 2.8V$$

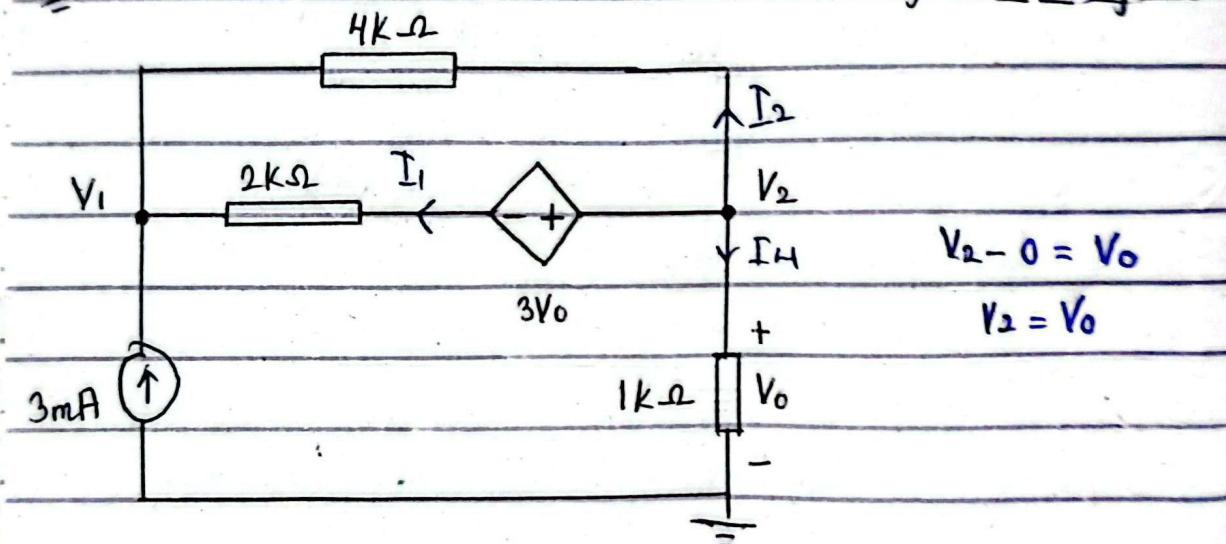Q. For the circuit below, find V_1 and V_2 using nodal analysis



- If there is a voltage source and a resistor connected in series between two nodes, then it is NOT a supernode.

Applying KCL at node-1 :-

$$\sum I_{\text{ent}} = \sum I_{\text{leav}}$$

$$3m + I_2 + I_1 = 0$$

$$3m + \left(\frac{V_2 - V_1}{4k} \right) + \left(\frac{V_2 - 3V_0 - V_1}{2k} \right) = 0$$

$$(12m + 6V_0 + 4V_1) / 12k = 0$$

$$\Rightarrow 4(3m) + V_2 - V_1 + 2V_2 - 6V_0 - 2V_1 = 0$$

$$4(3m) + V_2 + 2V_2 - V_1 - 2V_1 - 6V_0 = 0$$

$$\Rightarrow 12m + V_2 + 2V_2 - V_1 - 2V_1 - 6V_0 = 0$$

$$\Rightarrow 12 + 3V_2 - 3V_1 - 6V_0 = 0$$

$$12 + 3V_2 - 3V_1 - 6V_0 = 0$$

$$12 + 3V_2 - 6V_2 - 3V_1 = 0$$

$$12 - 3V_2 - 3V_1 = 0$$

$$-3V_1 - 3V_2 + 12 = 0$$

$$-3(V_1 + V_2 - 4) = 0$$

$$V_1 + V_2 - 4 = 0 \quad \text{--- (1)}$$

Applying KCL at node-2 :-

$$\Rightarrow \sum I_{\text{ent}} = \sum I_{\text{leav}}$$

$$0 = I_A + I_2 + I_1$$

$$0 = \left(\frac{V_2}{1k} \right) + \left(\frac{V_2 - V_1}{4k} \right) + \left(\frac{V_2 - 3V_0 - V_1}{2k} \right)$$

$$0 = 4V_2 + V_2 - V_1 + 2V_2 - 6V_0 - 2V_1$$

$$0 = 4V_2 + V_2 + 2V_2 - 6V_2 - 2V_1 - V_1$$

$$0 = V_2 - 3V_1$$

$$\Rightarrow -3V_1 + V_2 = 0 \quad -3V_1 + V_2 = 0$$

$$(V_1 + V_2 = 4) \times -1 \Rightarrow +V_1 - V_2 = -4$$


$$\Rightarrow -3(1) + V_2 = 0 \quad -4V_1 = -4$$

$$-3 + V_2 = 0 \quad V_1 = 1V$$


$$V_2 = 3V$$

$$\therefore V_1 = 1V$$

$$V_2 = 3V$$

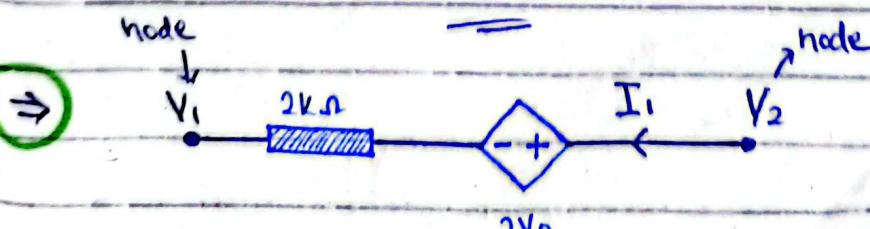
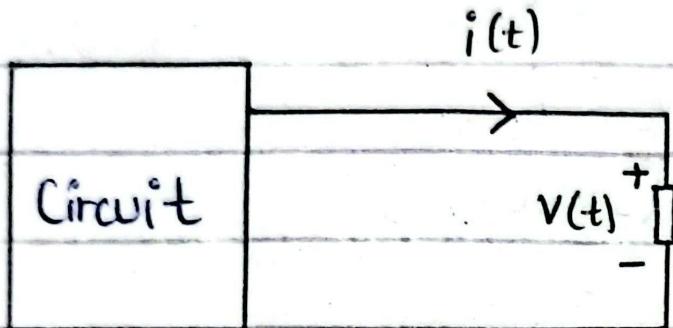
$$\Rightarrow \frac{V_2 - 3V_0 - V_1}{2k} = I_1$$



The current, by the
passive sign convention
enters the positive terminal
of the component ;


④ When the power is calculated;

- IF the value is +ve, then that element is absorbing power.
- IF the value is -ve, then that element is supplying power.

⑤ If an element is supplying power, then the current
LEAVES the positive (+ve) terminal of the element.

IDEAL Op AMP

neg. controlled
voltage source.

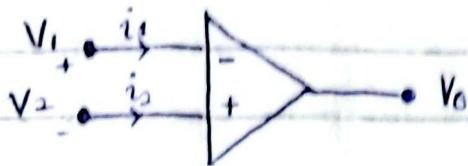


Assumptions of an ideal op-amp :

$\Rightarrow i_1 \text{ and } i_2 \approx 0$

$\Rightarrow V_1 \approx V_2$ (i.e. $V_d \approx 0$) } voltage difference is zero.

e.g. Rework using ideal op-amp model :

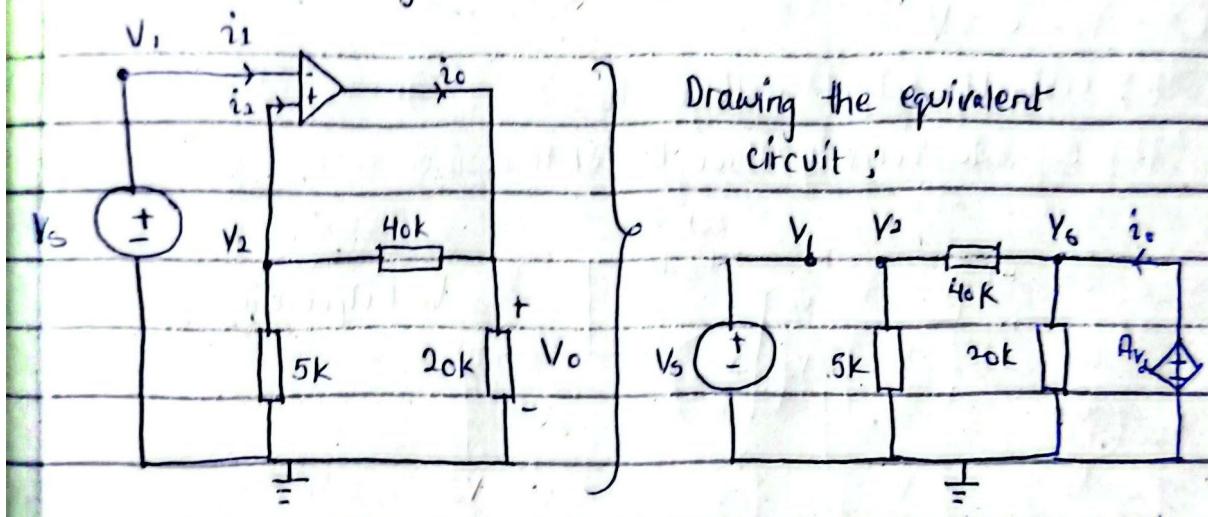

In an ideal op-amp configuration;

$$\Rightarrow V_3 = V_1$$

and since $V_1 \approx V_2$,

$$\therefore V_2 = V_3$$


Applying the voltage

divider rule :

$$\Rightarrow V_2 = V_0 \left(\frac{5k}{45k} \right) = \frac{9}{45} V_0$$

$$\Rightarrow \frac{V_0}{V_3} = 9$$

Inverting Amplifier

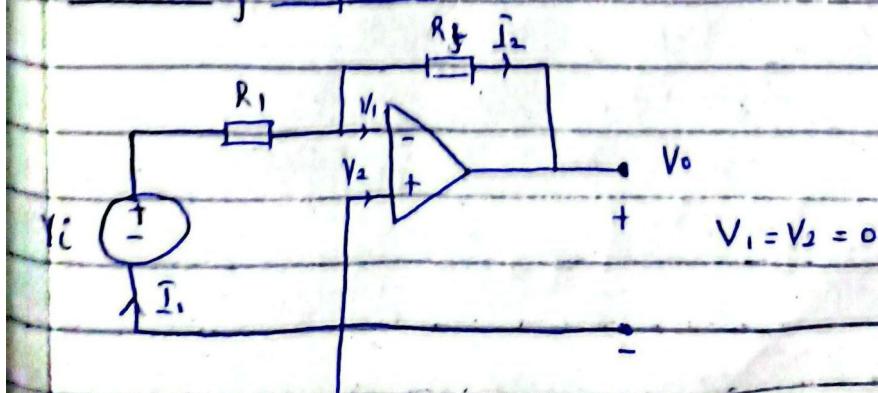

$$KCL: I_1 = I_2$$

$$\frac{V_i - 0}{R_1} = \frac{0 - V_o}{R_f}$$

$$\frac{V_o}{R_f} = -\frac{V_i}{R_1}$$


$$V_o = \left(-\frac{R_f}{R_1} \right) V_i$$

5.3

$$\text{e.g. } V_i = 0.5V$$

(a) Calculate output voltage V_o

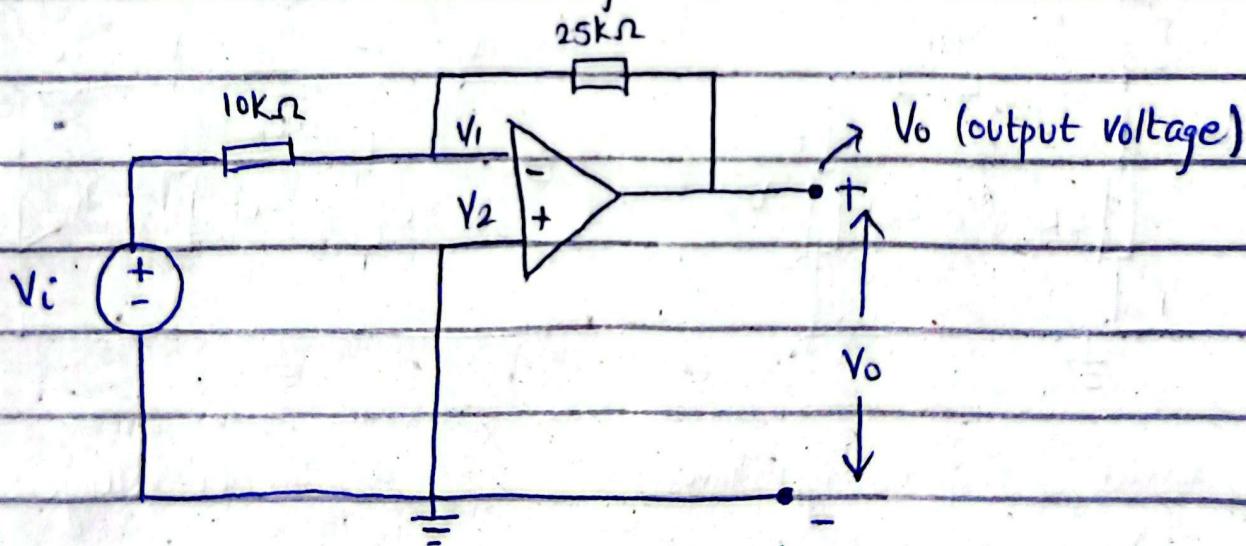(b) Calculate current through $10k\Omega$ resistor



$$\Rightarrow V_o = -\frac{R_f}{R_1} (V_i) = -\left(\frac{25}{10}\right)(0.5) = -2.5V$$


\Rightarrow Since the circuit is an IDEAL op-amp;

$$V_+ \approx V_- = 0$$

$$\frac{V_i - V_+}{10k} = i = \frac{V_i - 0}{10k} = \frac{0.5}{10k} = 50\mu A, = i$$

5.4

E-9 Determine V_o

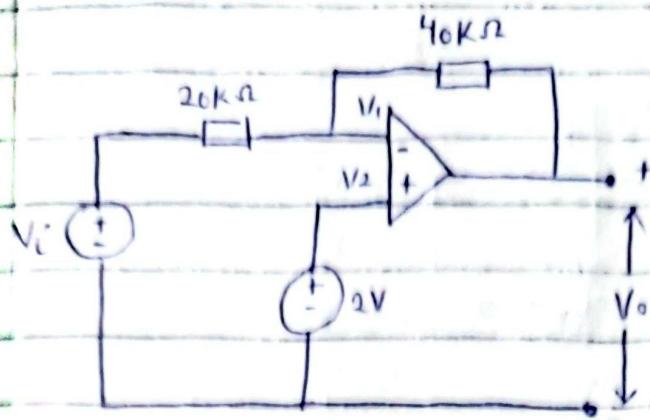

$$\Rightarrow V_i = 6V \text{ (given)}$$

In an ideal op-amp circuit; $V_1 \approx V_2$, and since V_1 is connected with the output voltage, V_o ; $\therefore V_1 = V_o$.

$$\Rightarrow \frac{6 - 2}{20k} = \frac{2 - V_o}{40k}$$


$$4(40k) = (20k)(2 - V_o)$$

$$160 = 40 - 20V_o$$

$$120 = -20V_o$$

$$V_o = -6V \text{ (non-inverting)}$$

Non-inverting amplifier

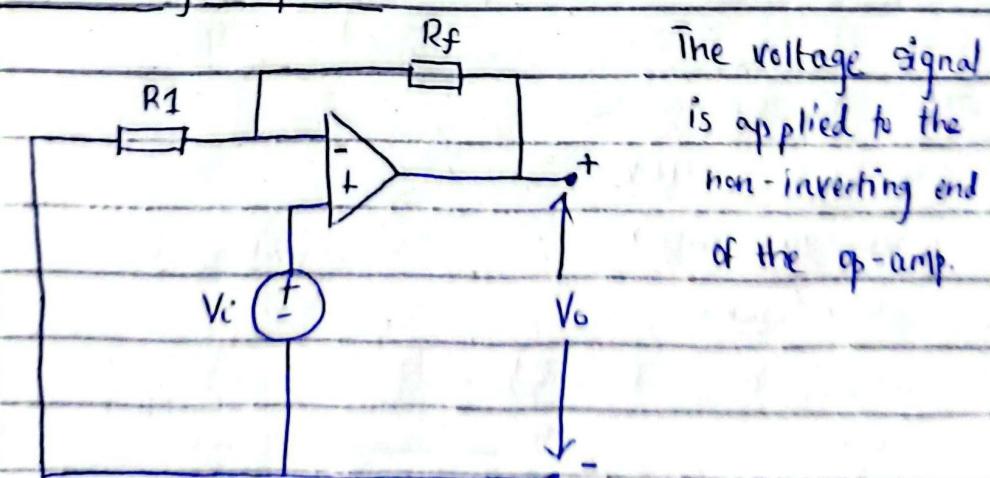

$$\therefore \text{In an ideal circuit; } \frac{0 - V_i}{R_1} = \frac{V_i - V_o}{R_f}$$


$$\Rightarrow V_1 = V_2 = V_i$$

$$\Rightarrow V_o = [1 + \frac{R_f}{R_1}] (V_i)$$

Any signal assigned at the non-inverting (+) end will positively amplify the signal.

PRACTICE PROBLEM 5.5

node-A

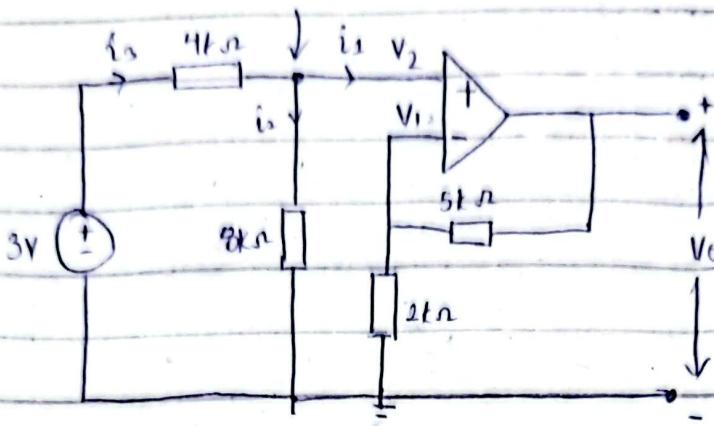

In an ideal circuit, $V_1 \approx V_2$.

Performing nodal analysis on node-A ;

$$\sum I_{\text{ent}} = \sum I_{\text{leav}}$$

$$\Rightarrow i_3 = i_2 + i_1$$

$$\frac{3 - V_A}{4K} = \left(\frac{V_A}{8K} \right) + \left(\frac{V_1}{2K} \right)$$

$$\frac{(3 - V_2)}{4K} = \left(\frac{V_2}{8K} \right) + \left(\frac{V_1}{2K} \right)$$

~~$$\frac{3 - V_2}{4K} = \frac{V_2}{8K} + \frac{4V_1}{8K}$$~~

$$\frac{3 - V_2}{4K} = \frac{V_2}{8K}$$

$$24K - 8KV_2 = 4KV_2$$

$$24K = 4KV_2 + 8KV_2$$

$$24K = 12KV_2$$

$$\frac{24000}{12000} = V_2 ; V_2 = 2V$$

$$\Rightarrow V_1 = V_2 = V_0 \left(\frac{2}{2+5} \right) = V_0 \left(\frac{2}{7} \right) = 2$$

$$\rightarrow V_0 (2) = 14$$

$$\underline{V_0 = 7V}$$

In an ideal


case, the input

current = 0 A.

- 5.6, 5.6

- Differential amplifiers

Summing amplifier

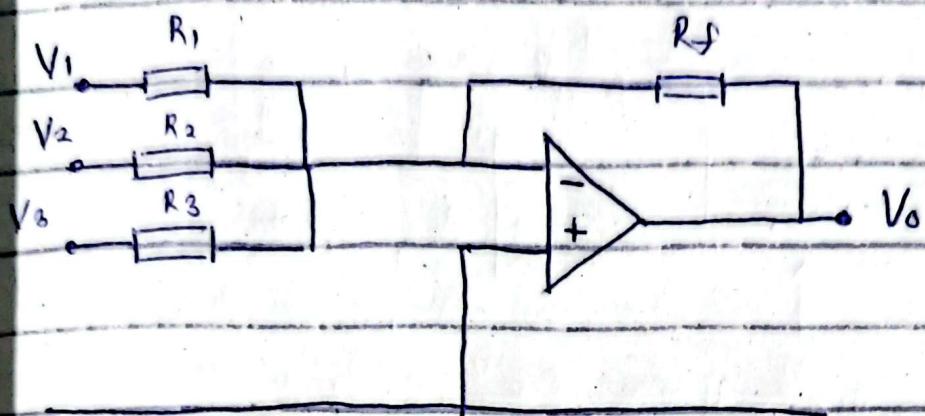

$$\Rightarrow V_0 = \left(-\frac{R_f}{R_1} \right) V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

IDCFI : $i_1 = 0, i_2 = 0, V_1 = V_2$

NON INVERTING : $V_0 = (1 + R_f/R_3)(V_1)$

INVERTING : $V_0 = (-R_f/R_3)(V_1)$

SUMMING : $V_0 = - \left(\frac{R_f (V_1)}{R_1} + \frac{R_f (V_2)}{R_2} + \frac{R_f (V_3)}{R_3} \right)$

$$\frac{V_0 + 5V_0}{10} = \frac{6V_0}{10} = \frac{6(-3)}{10} = -1.8$$

A capacitor is a voltage sensitive device \rightarrow resists instantaneous change of voltage.

Transient Circuits

Switches : Electrical component that brings about a change in the state of the circuit.



Normally open
switch



Normally closed
switch



Change over
switch

Transient state $\{t=0\}$

That state when the state of the circuit would change due to change in the position of the state.

Steady state $\{t=\infty\}$

When all changes due to change in the switch state die out.

\Rightarrow At a transient state ($t=0$), if the capacitor is uncharged, it will act as a short circuit ($V_C = 0$). [capacitor is voltage sensitive]

\hookrightarrow in the case of DC circuits.

assuming
capacitor is initially
uncharged

CAPACITIVE REACTANCE : $X_C = \frac{1}{j2\pi f C}$


For DC $f = 0$;

$X_C = \infty$ {In the steady state,
capacitor behaves as
open circuit}

INDUCTIVE REACTANCE : $X_L = j2\pi f L$

For DC $f = 0$;

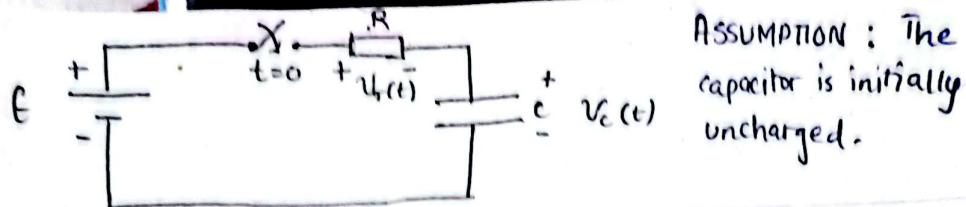$X_L = 0$ {In the steady state,
inductor behaves as
short circuit}



ASSUMPTION : The capacitor is initially uncharged.

At $t < 0$

$$i_c(0) = 0, V_c(0) = 0 \quad \} \text{ since switch was open}$$

At $t = 0$

$$i_c(0) = \frac{E}{R}, V_c(0) = 0 \quad \} \text{ transient state}$$

At $t > 0$

$$E = V_R(t) + V_C(t)$$

$$E = R i(t) + \frac{1}{C} \int i(t) dt$$

Taking derivative wrt time on both sides;

$$\frac{dE}{dt} = R \frac{di(t)}{dt} + \frac{1}{C} i(t)$$

Since there is no change in the direct voltage in a DC circuit ;

$$\frac{d i(t)}{dt} + \frac{1}{RC} i(t) = 0 - (1)$$

\Rightarrow General form of sol. for (1)

$$i(t) = \underbrace{A e^{mt}}_{\text{complementary sol.}} + \underbrace{k}_{\text{particular sol.}}$$

Since (1) is homogenous so particular sol. = 0 ;

$$\text{so } i(t) = A e^{mt} - (2)$$

Substituting (3) in (2) ;

$$\text{Let } m = \frac{d}{dt} \ln$$

$$i(t) = A e^{(\frac{-1}{RC})t}$$

To find A, we use initial

$$m i(t) + \frac{1}{RC} i(t) = 0$$

conditions ($t=0$) ;

$$i(0) = A e^0 = A = E/R$$

$$m = -\frac{1}{RC} - (3) \quad \dots$$

$$\therefore i(t) = \frac{E}{R} e^{-t/RC}$$

$$V_R(t) = R i(t) = E e^{-t/RC}$$

$$i(t)$$

10

one energy storage \rightarrow first order device circuit

$$V_c(t) = \frac{1}{C} \int i(t) dt + Rk$$

$$V_c(t) = \frac{1}{C} \int \frac{t}{R} e^{-t/RC} dt + kR = \frac{E}{RC} \times (RC) \cdot e^{-t/RC} + k$$

$$V_c(t) = R - Ee^{-t/RC}$$


@ initial conditions; $t=0$;

$$V_c(0) = R - Ee^0$$


$$0 = R - E$$

$$R = E$$
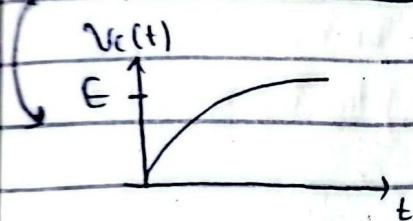
$$\therefore V_c(t) = E [1 - e^{-t/RC}]$$



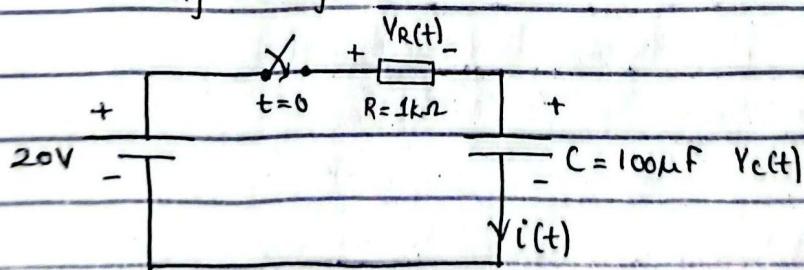Q. Find $i(t)$, $V_R(t)$, $V_c(t)$ for the given circuit when switches closes at $t=0$. Assume the capacitor is initially uncharged :-



At $t < 0$

$$i(0) = 0, V_c(0) = 0$$

At $t = 0$

$$i(0) = \frac{E}{R} = \frac{20}{1 \times 10^3} = 20mA, V_c(0) = 0$$

At $t > 0$

$$E = R i(t) + \frac{1}{C} \int i(t) dt$$

time dependent relationship between
voltage and current

$$V = L \frac{di}{dt}$$

} voltage across an
inductor

where V = instantaneous voltage across the inductor

L = inductance in Henrys

$\frac{di}{dt}$ = Instantaneous rate of current change

$$V(t_2) - V(t_1) = \frac{1}{C} \int_{t_1}^{t_2} i(t) dt$$

} voltage across a
capacitor

⇒ displaying a time dependent relationship between voltage
and current.


STEADY-STATE BEHAVIOR IN DC CIRCUITS

for circuits consisting of DC sources, resistors, capacitors, inductors
and switches, etc;


- ⇒ If all the switches all remain in a given state "for a long time...":
 - ⇒ Inductors will behave like short circuits.
 - ⇒ Capacitors will behave like open circuits.
 - ⇒ Steady-state behavior (in most cases $t(0^+)$) can be determined by applying the above two types of substitutions and analyzing the circuit.

If two ends of a resistor are connected to the same node, and essentially, there is zero resistance path, and therefore, no current will flow through the resistor.

e.g. →

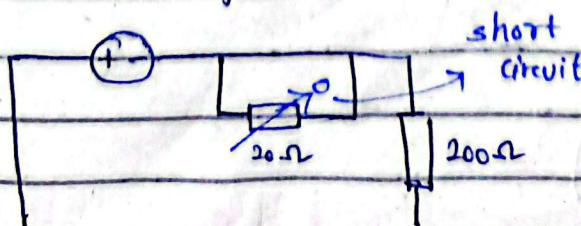


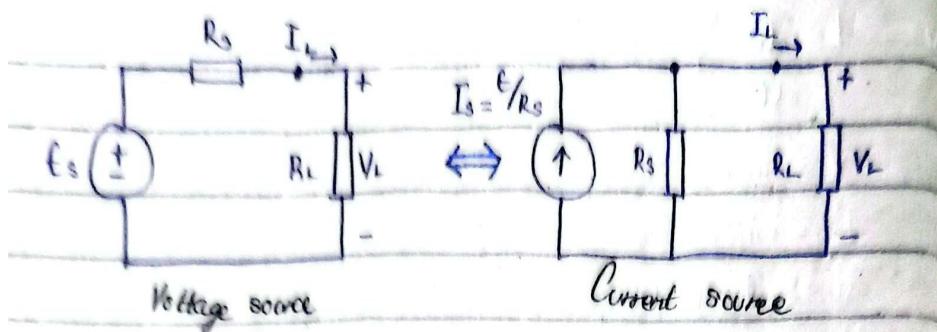Amongst the many techniques that can be applied, source transformation(s) is one of them.




- $\epsilon_s = I_s R_s$ } when converting a current source in \parallel with resistor
- $I_s = \epsilon_s / R_s$ } when converting a voltage source in series with resistor

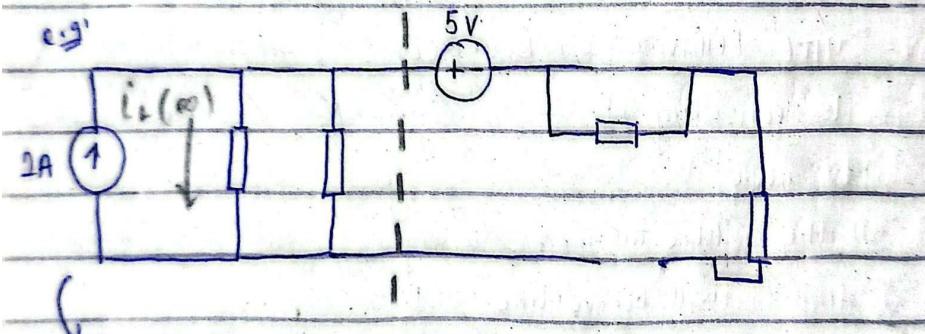① If a voltage source is connected in series with an open circuit (a gap with infinite resistance, $R = \infty$), the current = 0 through every series component, including the voltage source itself.



As time goes infinite, no current will flow in the right half of the circuit.

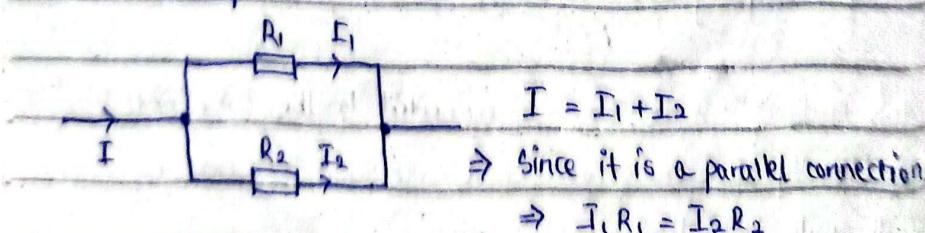Another technique that can be used is current division.



$$\Rightarrow I_1 = I \left(\frac{R_2}{R_1 + R_2} \right)$$


$$\Rightarrow I_2 = I \left(\frac{R_1}{R_1 + R_2} \right)$$

Since :

- $V_L(t) = L \frac{di}{dt}$
- $i_C(t) = C \frac{dv}{dt}$

Current cannot change instantly through an inductor and voltage cannot change instantly in a capacitor.

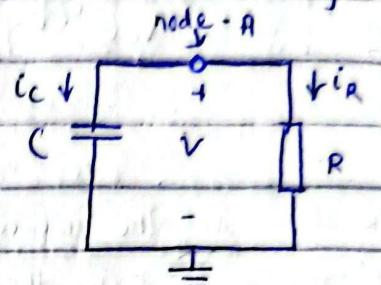- A source-free RC circuit occurs when its DC source is suddenly disconnected. The energy already stored in the capacitor is released to the resistors.
- ⇒ Consider a series combination of a resistor and an initially charged capacitor;



Since the capacitor is initially charged, we can assume that at time $t = 0$, the initial voltage is :

$$V(0) = V_0$$

with the corresponding value of the energy stored as :

$$W(0) = \frac{1}{2} CV_0^2$$

Applying KCL at the top node (node - A) yields :

$$i_C + i_R = 0$$

By definition, $i_C = C \frac{dv}{dt}$ and $i_R = V/R$. Thus,

$$C \frac{dv}{dt} + V/R = 0$$

$$\Rightarrow \frac{dv}{dt} + \frac{V}{RC} = 0$$

This is a first-order differential equation, since only the first derivative of v is involved.

To solve it, we rearrange the terms as :

$$\frac{dv}{v} = -\frac{1}{RC} dt$$

Integrating both sides, we get :

$$\ln v = -t/RC + \ln A \quad \text{In A is the integration constant}$$

Taking powers of e produces

$$v(t) = Ae^{-t/RC}$$

⇒ From the initial conditions, $v(0) = A = V_0$.

$$\therefore v(t) = V_0 e^{-t/RC}$$


⇒ The above scenario assumes that there is no voltage source.

→ [CONTINUOUS FROM LAST PAGE]

This shows that the voltage response of the RC circuit is an exponential decay of the initial voltage.

In terms of the time constant,

$$V(t) = V_0 e^{-t/\tau}$$

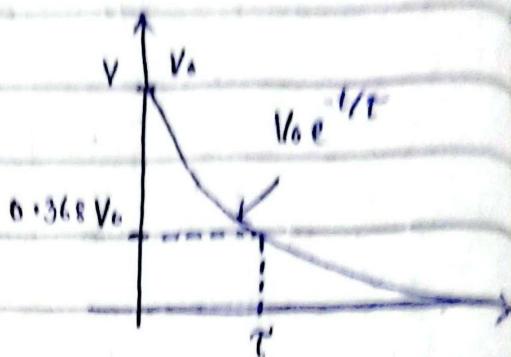

- The smaller the time constant, the more rapidly the voltage decreases, that is, the faster the response.

A circuit with a small time constant gives a fast response in that it reaches the steady state (or final state) quickly due to quick dissipation of energy stored.

⇒ With the voltage, $V(t)$, the current $i_R(t)$ can be found:

$$i_R(t) = \frac{V(t)}{R} = \frac{V_0 e^{-t/\tau}}{R} \quad \left. \begin{array}{l} \text{current through} \\ \text{the resistor} \end{array} \right\}$$

⇒ The power dissipated through the resistor up to time t is:

$$\cancel{p(t) = V(t) i_R(t) = (V_0 e^{-t/\tau}) \left(\frac{V_0 e^{-t/\tau}}{R} \right) = \frac{V_0^2 e^{-2t/\tau}}{R}}$$

$$\therefore p(t) = \frac{V_0^2 e^{-2t/\tau}}{R}$$

Q1.

Refer to the circuit in fig. 7.7.

Let $V_C(0) = 60V$. Determine

V_C , V_x , and I_c for $t \geq 0$.


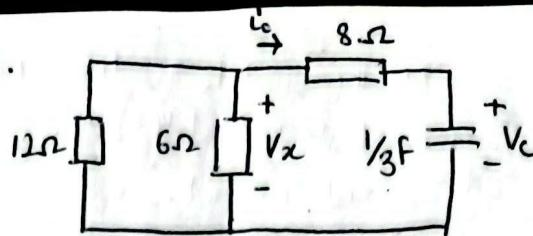


fig 7.7

At time $t=0$; $V_C(0) = 60V$.

→ finding the equivalent resistance, or, the Thevenin resistance at the capacitor terminals;
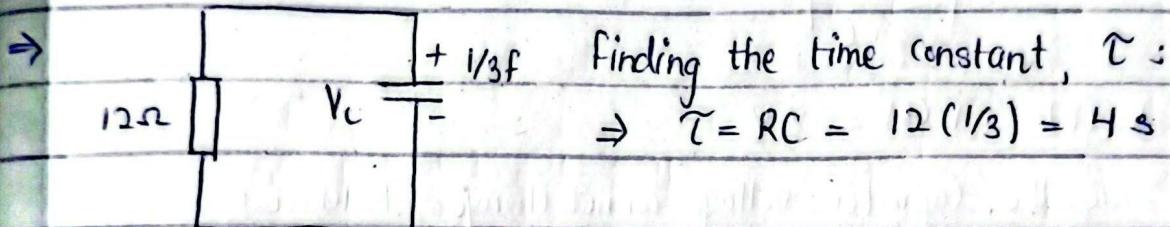
$$\frac{12(6)}{12+6} = \frac{72}{18} = 4; 4 + 8 = 12\Omega$$



→ Thus, the voltage stored across the capacitor for $t \geq 0$ is ;

$$V(t) = V_C(0)e^{-t/\tau} = 60e^{-0.25t} V$$

→ Since voltages are same in parallel circuits, and only currents are different ; (Voltage of V_x is the same one across the 12Ω resistor)

$$V_x = (60e^{-0.25t}) \left(\frac{4}{4+8} \right) = (60e^{-0.25t})(1/3) = 20e^{-0.25t}$$

$$\therefore V_x = 20e^{-0.25t} V \quad \text{through voltage division}$$

→ Applying voltage division to find the voltage across the 8Ω resistor :

$$V_{8\Omega} = (60e^{-0.25t}) \left(\frac{8}{4+8} \right) = 40e^{-0.25t} V$$

$$V = IR; I = V/R = 40e^{-0.25t}/8 = 5e^{-0.25t} A$$

Q2.

If the switch in fig. 7.10 opens at $t=0$, find $V(t)$ for $t \geq 0$, and $w_c(0)$.

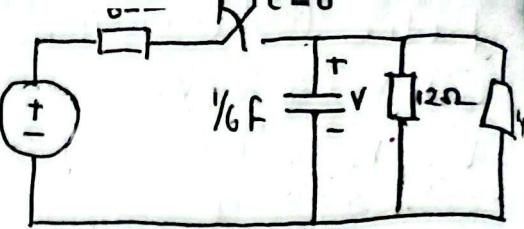


Fig 7.10.

For $t < 0$, the switch was closed.

∴ The capacitor acts as an open circuit to DC steady state.

$$\Rightarrow \frac{12(4)}{12+4} = \frac{48}{16} = 3\Omega$$

Using voltage division ;

$$\Rightarrow V_{ii} = 24 \left(\frac{3}{3+6} \right) = 8V ; t < 0$$

$$\Rightarrow V_C(t) = V(t) = 8V$$

∴ Since the capacitor voltage cannot change instantaneously, the voltage calculated at $t=0^-$ is equal to the voltage at $t=0^+$, or ;

$$\Rightarrow V_C(0) = V_0 = 8V$$

for $t \geq 0$, the switch is opened ;

The left half of the circuit is essentially discarded, since no current flows in that :

finding the time constant, $\tilde{\tau}$;

$$\left. \begin{array}{c} \frac{1}{6}F \\ | \\ -V \\ | \\ 12\Omega \\ | \\ 4\Omega \end{array} \right\} \Rightarrow \tilde{\tau} = RC = (12)(4)(\frac{1}{6}) = (3)(\frac{1}{6}) = 0.5s$$

Thus, the voltage across the capacitor for $t \geq 0$ is :

$$V(t) = V_C(0) e^{-\frac{t}{\tilde{\tau}}} = 8 e^{-\frac{t}{0.5}} = 8 e^{-2t} V$$

The initial energy stored in the capacitor is :

$$\Rightarrow W_C(0) = \frac{1}{2} C V_C(0)^2 = \frac{1}{2} (\frac{1}{6})(8)^2 = 5.333 J$$

■ SOURCE-FREE R - L CIRCUIT

\hookrightarrow circuit response = current $i(t)$ through the inductor

\Rightarrow When a circuit has a single inductor and several resistors and dependent sources, the THEVENIN equivalent can be found at the terminals of the inductor to form a simple RL circuit.

\Rightarrow Current enters the positive (+ve) side.

Current leaves the negative (-ve) side.

$$i(t) = i(0) e^{-t/R} \quad ; \quad R = L/C$$


Q. In the circuit shown in Fig. 7.19

find v_o and i for all time,

assuming that the switch was open $10V$


for a long time :

For $t < 0$, the switch was open :

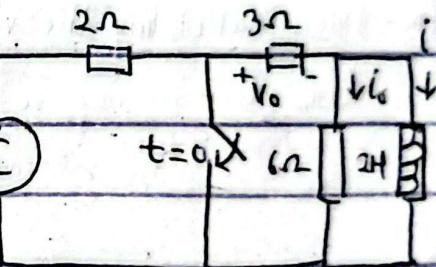

The inductor acts like a short circuit in the DC steady state;

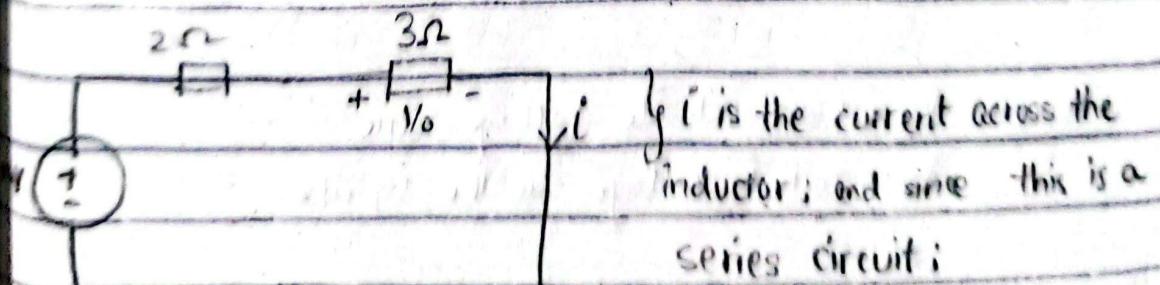- the 6Ω is also short circuited, since the current takes the path of least resistance; $i_0 = 0 \quad ; \quad t < 0$



$$\therefore i_0 = i(2+3) = i(t); \quad i = 2A; \quad t < 0$$


$$v_o = 10 \left(\frac{3}{3+2} \right) = \frac{30}{5} = 6V; \quad t < 0 \quad \begin{cases} \text{using voltage} \\ \text{division} \end{cases}$$

for $t > 0$, the switch is closed;

\Rightarrow The wire, where the switch is, short circuits the voltage source, in series with the resistor;

3Ω and 6Ω are in parallel

\Rightarrow

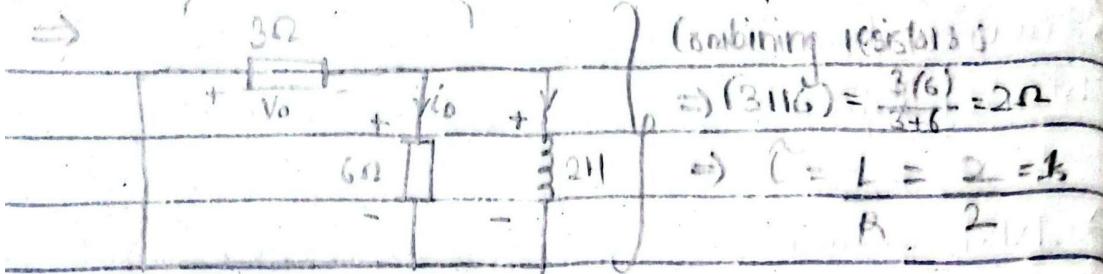

$$\therefore i = i(0)e^{-t/R} = 2e^{-t/2} \text{ A } ; t > 0$$

\Rightarrow Since the inductor is in parallel with the 6Ω and the 3Ω resistor;

$$\therefore V_{2H} = -V_{3H} = -V_0 = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t}$$

$$V_0 = 4e^{-t} \text{ V. } ; t > 0$$

$$\Rightarrow V = IR \text{ ; } V/R = I \text{ ; } i_0 = \frac{4e^{-t}}{6} = -\frac{2}{3}e^{-t} \text{ A. } ; t > 0$$

① When calculating the voltage of the inductor; $V(t) = L \frac{di}{dt}$;

the $\frac{di}{dt}$ is negative (-ve), since the current after $t > 0$, is on $\frac{dt}{dt}$ exponential decay (decreasing).

Assuming the capacitor is initially charged; with a initial voltage, V_0 .

$$\Rightarrow V(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-t/C} & t > 0 \end{cases}$$

where V_s = constant dc voltage source

V_0 = initial voltage on the capacitor

If we assume that the capacitor is initially uncharged, then,

$$V_0 = 0;$$

$$\Rightarrow V(t) = \begin{cases} 0 & t < 0 \\ V_s(1 - e^{-t/C}) & t > 0 \end{cases}$$

Complete response = TRANSIENT RESPONSE + STEADY-STATE RESPONSE
 (temporary part) (permanent part)


$$\Rightarrow V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

where $V(0)$ = initial capacitor voltage

$V(\infty)$ = final capacitor voltage

τ = time constant

When $t = 00$ s

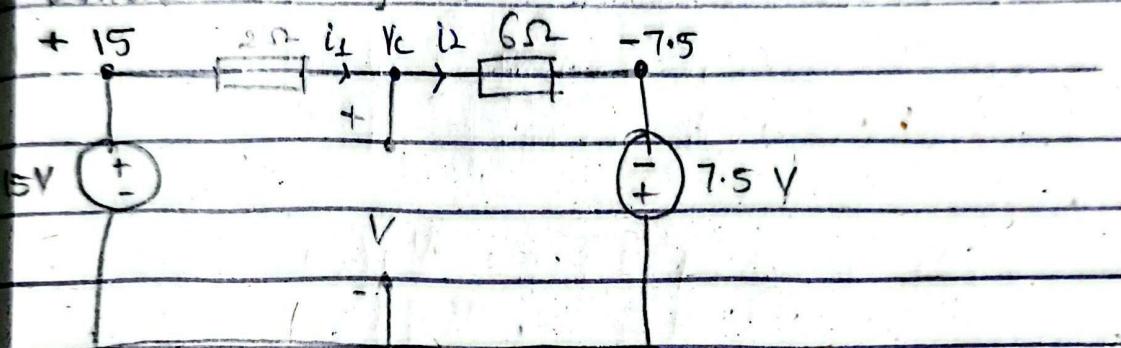

Applying KCL at node V_C :

$$\Rightarrow i_1 = i_2$$

$$\frac{5 - V_C}{2} + \frac{V_C}{6} = V_C - (-7.5) = V_C + 7.5$$

$$\Rightarrow \frac{\frac{15 - V_C}{2} - \frac{V_C}{6}}{X} = V_C + 7.5$$

$$90 - 6V_C - 9V_C = 2V_C + 15$$

$$-15V_C / -7V_C = 45 + 90$$

$$90 - 15 = 2V_C + 6V_C$$

$$75 = 8V_C$$

$$\therefore V_C = 9.375 \text{ V}$$

For the step response of an RL circuit:

$$\Rightarrow i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$