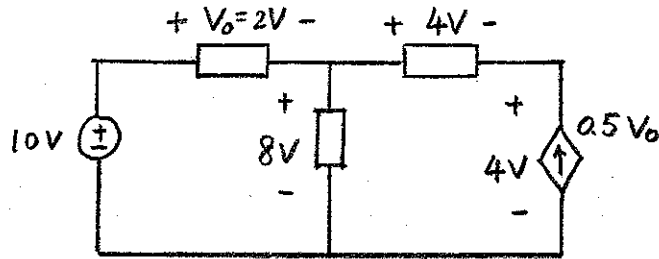


Name: _____

Last 4 digits of ID: _____

1. In the circuit below, find the power associated with the dependent source.



2. Figures below show the current through and voltage across a device.

(a) sketch the power delivered to the device for $t > 0$.

(b) find the total energy absorbed by the device for $0 < t < 4$ s.

