

**ELECTRICAL ENGINEERING DEPARTMENT
CALIFORNIA POLYTECHNIC STATE UNIVERSITY**

EE 112 Electric Circuit Analysis I

FINAL EXAM

Winter 2004


Name: _____ Last 4 digits of Student ID: _____

Section #: _____

1 (20)	2 (20)	3 (15)	4(15)	5 (15)	6(15)	Total (100)

PROBLEM #1

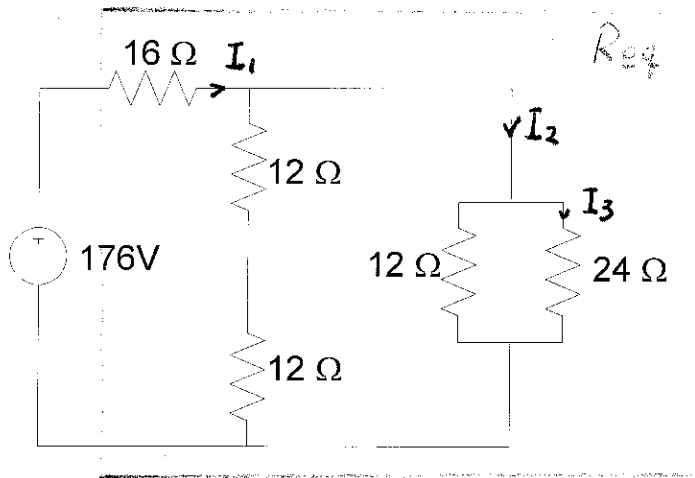- (a) Find the power supplied by the voltage source and the power absorbed by the 24 Ω resistor in the following figure.
 (b) Repeat (a) if the 176 V source is increased to 300 V.



$$(a) \quad R_{eq} = 16 + (12 + 12) \parallel (12 \parallel 24) = 16 + 24 \times \frac{12 \times 24}{12 + 24} = 22 \Omega$$

$$I_1 = \frac{176}{R_{eq}} = 8 \text{ A}$$

$$\text{Using current division: } I_2 = \frac{24}{24 + 8} \cdot I_1 = 6 \text{ A}, \quad I_3 = \frac{12}{12 + 24} \cdot I_2 = 2 \text{ A}$$

$$P_{24\Omega} = I_3^2 \cdot R = 2^2 \times 24 = 96 \text{ W}$$

$$P_{176V} = -VI_1 = -176 \times 8 = -1408 \text{ W}$$

(b) Using linearity Property

$$\tilde{I}_1 = k \cdot I_1, \text{ where } k = \frac{300}{176} = 1.704$$


$$\tilde{I}_3 = k \cdot I_3$$

$$\therefore \tilde{P}_{24\Omega} = \tilde{I}_3^2 \cdot R = (1.704 \times 2)^2 \times 24 = 279 \text{ W}$$


$$\tilde{P}_{300V} = -300 \tilde{I}_1 = -300 \times 1.704 \times 8 = -4090.9 \text{ W}$$

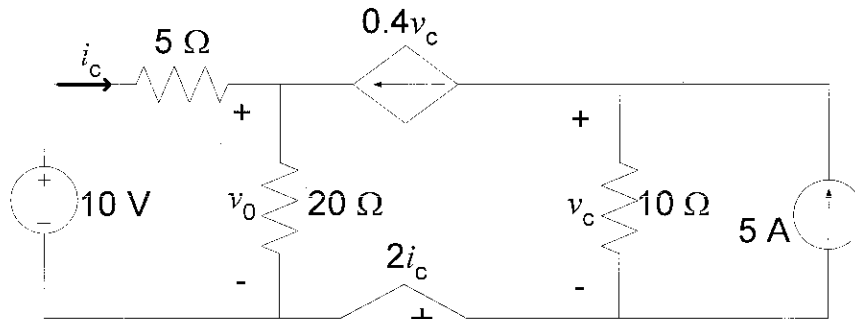PROBLEM #2

Use the principle of superposition to find v_o and power absorbed by the 20Ω resistor.



5 A acting alone:

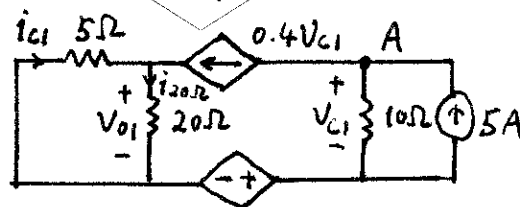

Apply KCL @ node A:


$$5 - \frac{v_{c1}}{10} - 0.4v_{c1} = 0$$

$$0.5v_{c1} = 5 \Rightarrow v_{c1} = 10V$$

$$i_{20\Omega} = 0.4v_{c1} \cdot \frac{5}{5+20} = 4 \times \frac{1}{5} = 0.8A$$

$$v_{o1} = 20 \cdot i_{20\Omega} = 16V$$

10V acting alone:

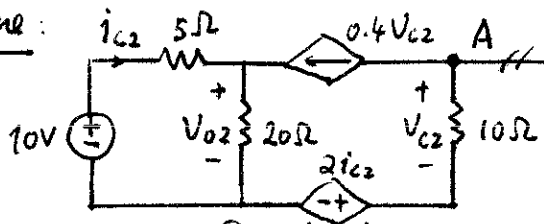

Apply KCL @ node A:

$$+0.4v_{c2} + \frac{v_{c2}}{10} = 0 \Rightarrow v_{c2} = 0V$$

$$v_{o2} = 10 \cdot \frac{20}{20+5} = 8V$$

$$v_o = v_{o1} + v_{o2} = 16 + 8 = 24V$$

$$P_{20\Omega} = v_o^2 / R = 24^2 / 20 = 28.8W$$

Note:


the same results can be obtained by using standard mesh analysis + eq. for controlled sources.

However don't (!) attempt to write KVL eq. for the mesh containing \diamondleftarrow , or ignore the voltage drop across \diamondleftarrow !!!

The mesh current in the mesh with \diamondleftarrow equals $-0.4v_{c1}$.

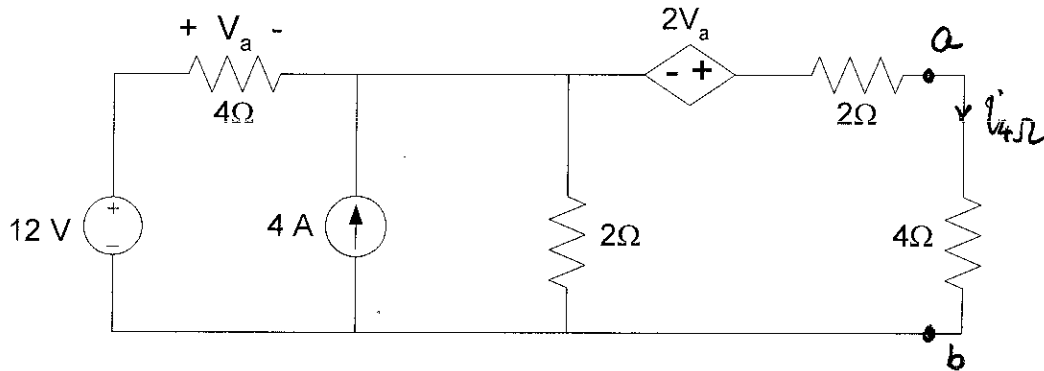
PROBLEM #3

Use Norton's theorem to determine the current flowing through the right-hand $4\ \Omega$ resistor in the figure below.



Find the Norton equivalent left to a-b :

1. R_{eq} :

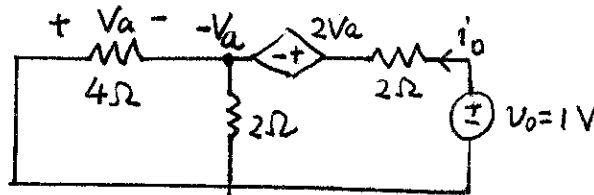


$$\text{nodal eq. for } -V_a: \quad -\frac{V_a}{4} - \frac{-V_a}{2} + \frac{1 - (-V_a + 2V_a)}{2} = 0$$

$$+V_a + 2V_a + 2 - \frac{1}{2}V_a = 0 \rightarrow V_a = \frac{2}{3} \text{ V}$$

$$i_0 = \frac{1 - V_a}{2} = \frac{1 - 2/3}{2} = \frac{1}{6} \text{ A}$$

$$R_{eq} = V_0 / i_0 = 1 / (1/6) = 6\ \Omega$$

2. V_{oc} :

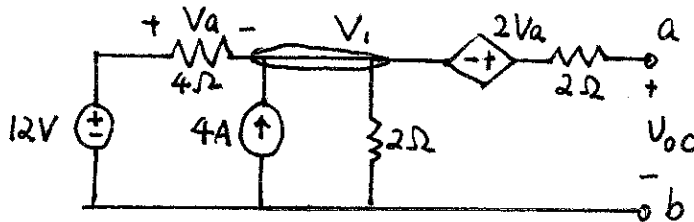

nodal eq. for V_1 :


$$\frac{12 - V_1}{4} + 4 - \frac{V_1}{2} = 0 \rightarrow 12 - V_1 + 16 - 2V_1 = 0 \rightarrow V_1 = \frac{28}{3} \text{ V}$$

$$V_a = 12 - V_1 = \frac{8}{3} \text{ V}$$

$$V_{oc} = 2V_a + V_1 = \frac{16}{3} + \frac{28}{3} = \frac{44}{3} \text{ V}$$

$$I_N = \frac{V_{oc}}{R_{eq}} = \frac{44/3}{6} = \frac{22}{9} \text{ A}$$

\therefore Norton equivalent:

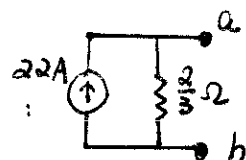


Using current division: $i_{4\Omega} = \frac{22/9}{6 + 4} = \frac{22}{90} \text{ A}$

note:
 $V_{oc} \neq V_1$
there is voltage drop
across \diamond !!!

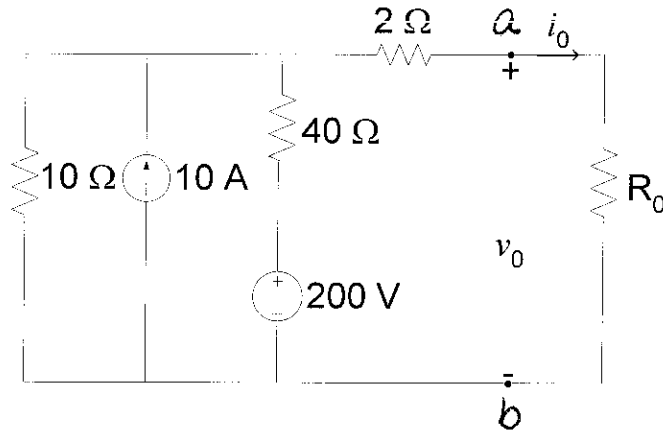
PROBLEM #4

Determine i_0 and v_0 in the following circuit when R_0 is 0, 2, 10, 20, and 50 Ω .




Find the Thevenin equivalent left to a-b :

1. R_{eq} :

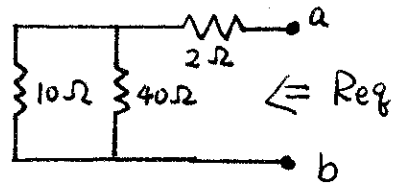

$$R_{Th} = R_{eq} = 10 \parallel 40 + 2 = 10 \Omega$$


2. V_{oc} :

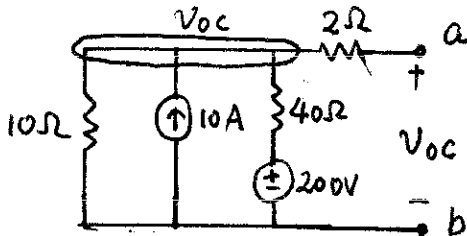

nodal eq. for V_{oc}

$$-\frac{V_{oc}}{10} + 10 + \frac{200 - V_{oc}}{40} = 0$$
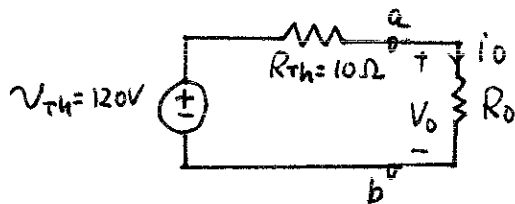
$$-4V_{oc} + 400 + 200 - V_{oc} = 0 \Rightarrow V_{oc} = 120V$$







$$i_0 = \frac{120}{10 + R_0}$$

$$v_0 = i_0 \cdot R_0$$


R_0	i_0 / A	v_0 / V
0 Ω	12	0
2 Ω	10	20
10 Ω	6	60
20 Ω	4	80
50 Ω	2	100

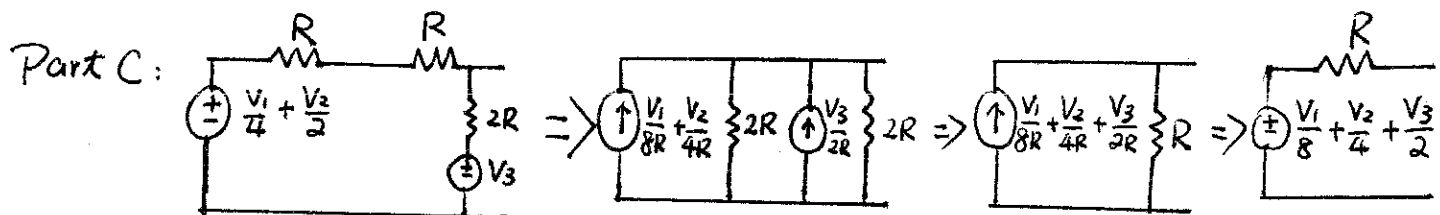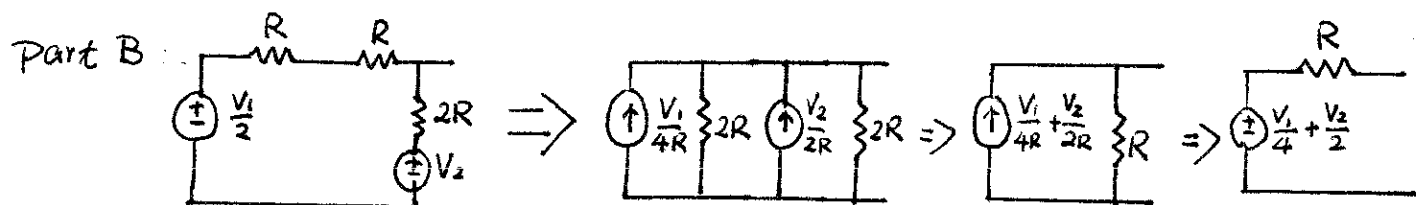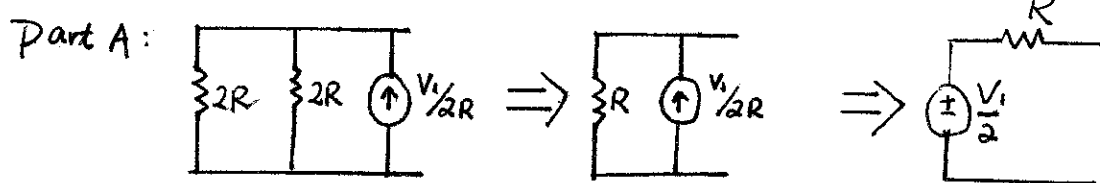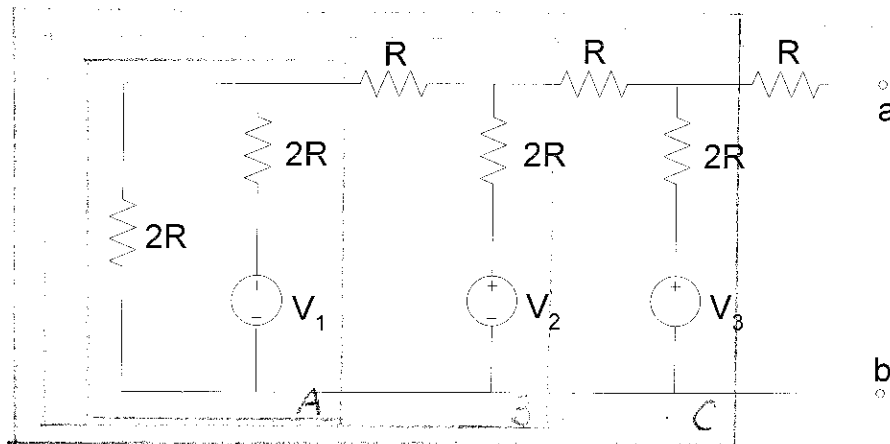PROBLEM #5

Find the Thevenin equivalent seen at a-b for the circuit below. (Hint: for this type of problem, the more natural solution technique is source transformation.)






the entire circuit left to a-b:

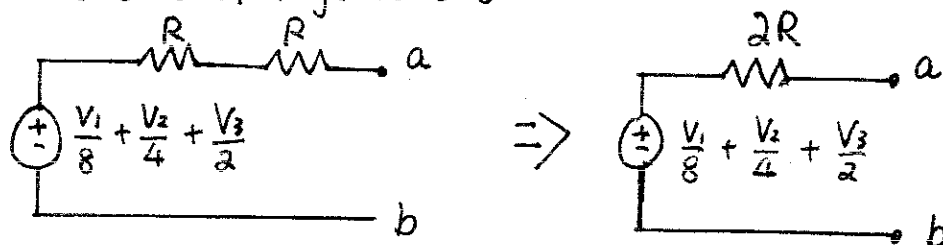

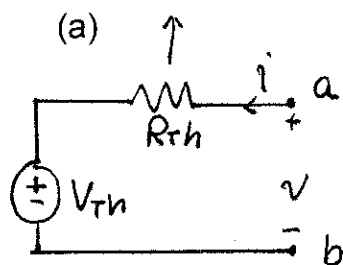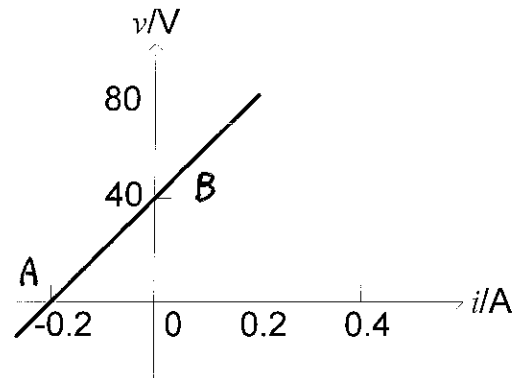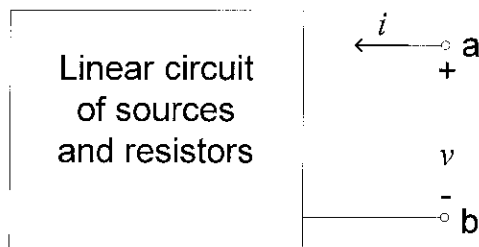PROBLEM #6

The linear resistive circuit in figure (a) is found experimentally to have the v - i relationship plotted in figure (b). Find the maximum power that can be absorbed by placing a load resistor across terminals a-b?



Apply KVL to the Thevenin equivalent:

$$-V_{Th} - iR_{Th} + v = 0$$

$$\Rightarrow v = iR_{Th} + V_{Th} \quad (1)$$

Find two points in (b)

A: $(-0.2A, 0V)$ substitute in (1)

B: $(0A, 40V)$

$$\begin{cases} 0 = -0.2R_{Th} + V_{Th} \\ 40 = 0 + V_{Th} \end{cases} \rightarrow \begin{cases} V_{Th} = 40V \\ R_{Th} = 200\Omega \end{cases}$$

Maximum power transfer occurs when

$$R_L = R_{Th} = 200\Omega$$

$$P_{L,max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{40^2}{4 \times 200} = \underline{2W}$$