



Lab report # 08

Submitted by: **Shayan Rizwan**

Registration Number: **2024585**

Submitted to: Engr. Irfanullah

Semester: 03

Faculty of Computer Science and Engineering
GIK Institute of Engineering Sciences and Technology

Task Statement:

Design a full adder using Behavioral modeling in Verilog, write test benches to verify its functionality, and simulate to visualize the waveforms and show its RTL.

Solution

CODE:

```
module
full_adder(a,b,c,carry,sum );

input a,b,c;

output sum,carry;

reg sum,carry;

always@( a or b or c)

begin

sum = a^b^c;

carry = (a&b) | c & (a^b);

end

endmodule
```

Test Bench:

```
` module full_adder_tb();

// Inputs

reg a;

reg b;

reg c;

// Outputs

wire sum;

wire carry;

full_adder
 uut(.sum(sum),.carry(carry),.a(a
),.b(b),.c(c));
```

```

initial
begin
    a = 0; b = 0; c=0;

    #10 a = 0; b = 0; c=1;

    #10 a = 0; b = 1; c=0;

    #10 a = 0; b = 1; c=1;

    #10 a = 1; b = 0; c=0;

    #10 a = 1; b = 0; c=1;

    #10 a = 1; b = 1; c=0;

    #10 a = 1; b = 1; c=1;


    $finish;

end


endmodule

```

RTL:

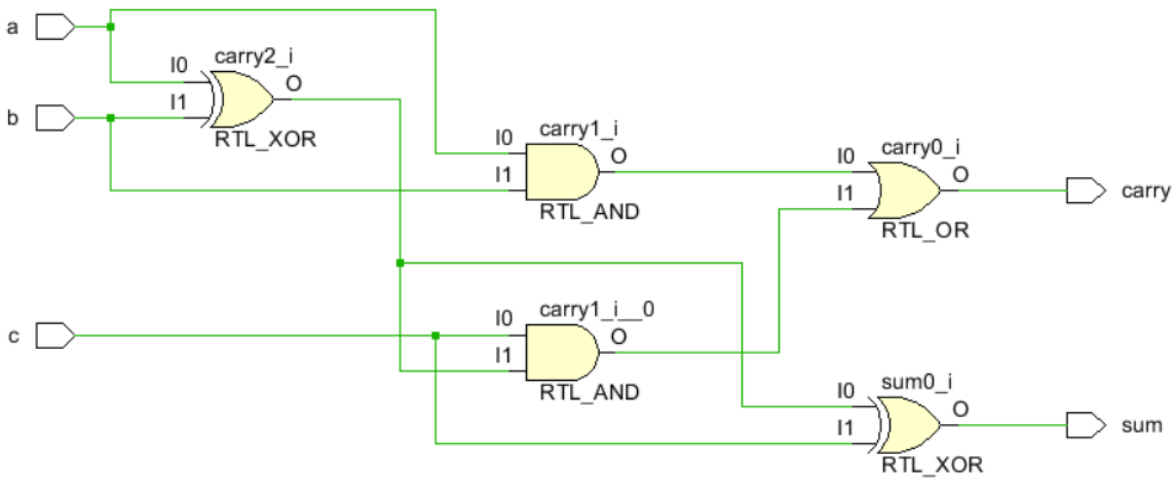

Output:

 

Task Statement:

Design a 4x1 Multiplexer using Behavioral modeling in Verilog, write test benches to verify its functionality, and simulate to visualize the waveforms and show its RTL.

Solution

Code

```
module mux_4x1(y,i,s);
output y;
input [3:0]i;
input [1:0]s;
reg y;
// Behavioural
always@(i or s)
// Using case statement
case(s)
3'b00:y = i[0];
3'b01:y = i[1];
3'b10:y = i[2];
3'b11:y = i[3];
default: y = 1'b0;
endcase
```

```
endmodule
```

Test Bench

```
module mux_4x1_tb();  
    // Inputs  
    reg [3:0] i;  
    reg [1:0] s;  
    // Outputs  
    wire y;  
    // Instantiate the Unit Under Test (UUT)  
    mux_8x1 uut ( .y(y),.i(i),.s(s));  
    initial  
    begin  
        // Initialize Inputs  
  
        i = 4'b1010;  
        s = 2'b00; #10;  
        s = 2'b01; #10;  
        s = 2'b10; #10;  
        s = 2'b11; #10;  
  
        i= 4'b1100;  
        s = 2'b00; #10;  
        s = 2'b01; #10;  
        s = 2'b10; #10;  
        s = 2'b11; #10;  
  
        i = 4'b0110;  
        s = 2'b00; #10;  
        s = 2'b01; #10;  
        s = 2'b10; #10;  
        s = 2'b11; #10;  
  
        i = 4'b1001;  
        s = 2'b00; #10;  
        s = 2'b01; #10;  
        s = 2'b10; #10;
```

```


s = 2'b11; #10;

i = 4'b1111;
s = 2'b00; #10;
s = 2'b01; #10;
s = 2'b10; #10;
s = 2'b11; #10;


i = 4'b0000;
s = 2'b00; #10;
s = 2'b01; #10;
s = 2'b10; #10;
s = 2'b11; #10;
$finish;
end
endmodule

```

RTL

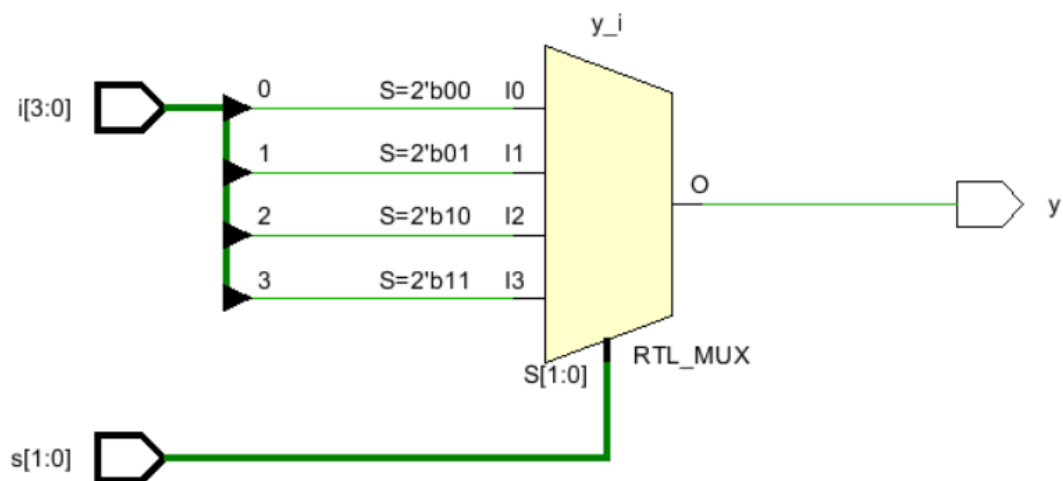

Output

 

Task Statement:

Design a 3x8 Decoder using Behavioral modeling in Verilog, write test benches to verify its functionality, and simulate to visualize the waveforms and show its RTL.

Solution

CODE:

```
module decoder_3x8(input [2:0] a,output reg [7:0] out,input en);
always @(*)
begin
if (en)
case(a)
3'b000: out = 8'b00000001;
3'b001: out = 8'b00000010;
3'b010: out = 8'b00000100;
3'b011: out = 8'b00001000;
3'b100: out = 8'b00010000;
3'b101: out = 8'b00100000;
3'b110: out = 8'b01000000;
3'b111: out = 8'b10000000;
default: out = 8'b00000000;
endcase
else
out = 8'b00000000;
end
```

```

end
endmodule


Test Bench:

module deocoder_3x8_tb();
reg [2:0] a;
reg en;
wire [7:0] out;
decoder_3x8 uut(.a(a),.en(en),.out(out));
initial
begin
$monitor($time, " a=%b, en=%b, out=%b", a, en, out);
en = 0;
a = 3'b000; #10;
a = 3'b001; #10;
a = 3'b010; #10;
a = 3'b011; #10;
a = 3'b100; #10;
a = 3'b101; #10;
a = 3'b110; #10;
a = 3'b111; #10;


en = 1;
a = 3'b000; #10;
a = 3'b001; #10;
a = 3'b010; #10;
    a = 3'b011; #10;
    a = 3'b101; #10;
    a = 3'b100; #10;
    a = 3'b110; #10;
    a = 3'b111; #10;
    $finish;
end
endmodule

```


RTL:

 

Output:

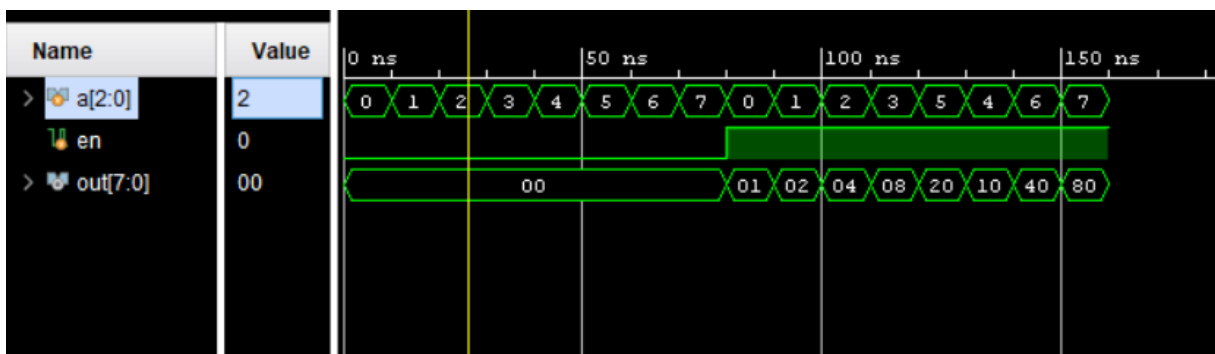

Task Statement:

Design an ALU using Behavioral modeling in Verilog, write test benches to verify its functionality, and simulate to visualize the waveforms and show its RTL.

Solution

Code:

```
module ALU(input [8:0] a,input [8:0] b,input [3:0] sel,output reg [8:0] c);
always @(*)
begin
case(sel)
```

```

4'b0000: c = a+b;
4'b0001: c = a-b;
4'b0010: c = a*b;
4'b0011: c = a&&b;
4'b0100: c = a||b;
4'b0101: c = a&b;
4'b0100: c = a|b;
4'b0111: c = a<<1;
4'b1000: c = a>>b;
4'b1001: c = ~a;
4'b1010: c = !a;
4'b1011: c = a+1;
4'b1100: c = a-1;
4'b1101: c = b+1;
4'b1110: c = b-1;
4'b1111: c = b;
endcase
end
endmodule

```

Test Bench:


```

module ALU_tb();
reg [8:0] a;
reg [8:0] b;
reg [3:0] sel;
wire [8:0] c;
ALU uut (.c(c),.a(a),.b(b),.sel(sel));
initial
begin
    a = 1;b = 1; sel = 4'b0000;
    #10  a = 1;b = 0; sel = 4'b0001;
    #10  a = 1;b = 1; sel = 4'b0010;
    #10  a = 1;b = 1; sel = 4'b0011;
    #10  a = 0;b = 1; sel = 4'b0100;
    #10  a = 1;b = 0; sel = 4'b0101;
    #10  a = 1;b = 1; sel = 4'b0110;

```

```
#10  a = 1;b = 1; sel = 4'b0111;  
#10  a = 1;b = 1; sel = 4'b1000;  
#10  a = 0;b = 1; sel = 4'b1001;  
#10  a = 1;b = 0; sel = 4'b1010;  
#10  a = 1;b = 1; sel = 4'b1011;  
#10  a = 1;b = 0; sel = 4'b1100;  
#10  a = 0;b = 0; sel = 4'b1101;  
#10  a = 0;b = 1; sel = 4'b1110;  
#10  a = 0;b = 0; sel = 4'b1111;  
#10  
$finish;  
end  
endmodule
```

RTL

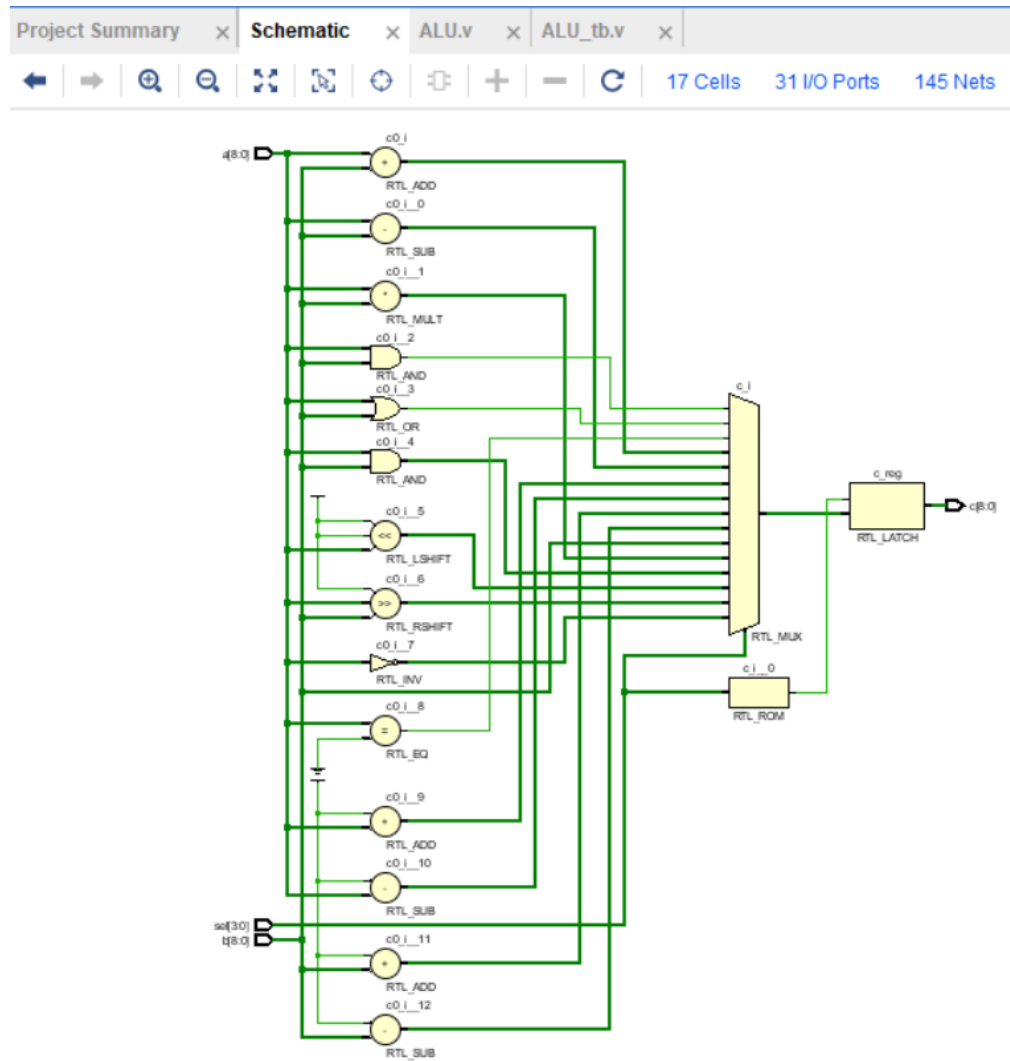

Output

