

CE211-L Circuit Analysis Lab



Lab Report # 5

Submitted by: **Syed Ali Hassan**

Registration Number: **2024616**


Submitted to: **Engr. Muhammad Shakaib**

Semester: **03**

Faculty of Computer Science and Engineering
GIK Institute of Engineering Sciences and Technology

Task Statement:

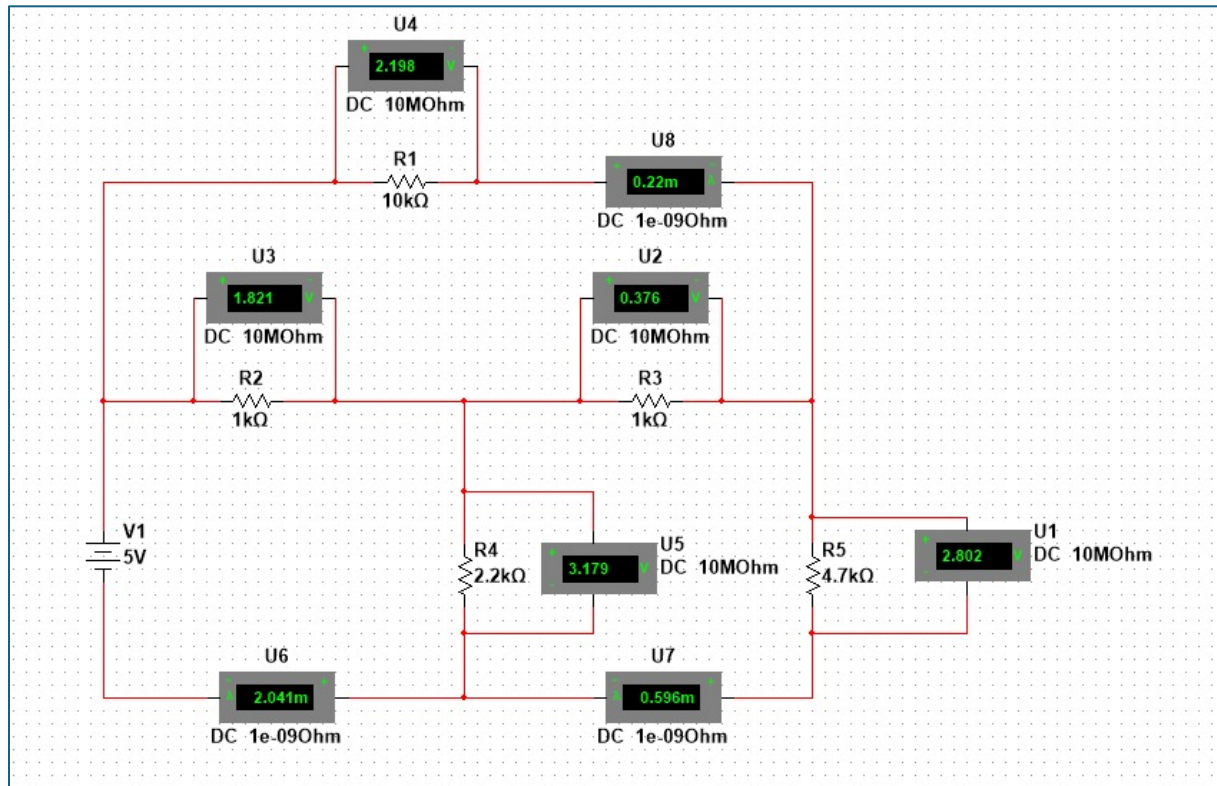1. Assemble the circuit in Figure with the component values shown in Table. Take measurements to complete the entries corresponding to the experimental values. (Hardware + Software)



Solution:

Resistor	Parameter	Theoretical	Experimental	% Error
10 k Ω	V_{r1}	2.200 V	2.196 V	0.18 %
1 k Ω	V_{r2}	1.821 V	1.843 V	1.19 %
1 k Ω	V_{r3}	0.376 V	0.38 V	1.05 %
2.2 k Ω	V_{r4}	3.179 V	3.19 V	0.32 %
4.7 k Ω	V_{r5}	2.802 V	2.812 V	0.36 %

Workings:

$$V = IR$$

$$\begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 3.2 & -2.2 & -1 \\ -2.2 & 7.9 & -1 \\ -1 & -1 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Det =

$$\Delta = 3.2 \begin{vmatrix} 7.9 & -1 \\ -1 & 12 \end{vmatrix} - (-2.2) \begin{vmatrix} -2.2 & -1 \\ -1 & 12 \end{vmatrix} - 1 \begin{vmatrix} -2.2 & 7.9 \\ -1 & -1 \end{vmatrix}$$
$$\Delta = 3.2[(7.9)(12) - (-1)(-1)] + 2.2[(-2.2)(12) - (-1)(-1)] - 1[(-2.2)(-1) - (7.9)(-1)]$$
$$\Delta = 229.78$$

$$\Delta x = 469.0$$

$$\Delta y = 137.0$$

$$\Delta z = 50.5$$

$$x = \frac{\Delta x}{\Delta} = 2.041$$

$$y = \frac{\Delta y}{\Delta} = 0.596$$

$$z = \frac{\Delta z}{\Delta} = 0.220$$

$$I_1 = 2.041, I_2 = 0.596, I_3 = 0.220$$

Apply Ohm's Law ($V=IR$)

$$V_{r1} = 10k (0.220) = \mathbf{2.20 \text{ V}}$$


$$V_{r2} = 1k (2.041 - 0.220) = \mathbf{1.821 \text{ V}}$$

$$V_{r3} = 1k (0.596 - 0.220) = \mathbf{0.376 \text{ V}}$$

$$V_{r4} = 2.2k (2.041 - 0.596) = \mathbf{3.179 \text{ V}}$$

$$V_{r5} = 4.7k (0.596) = \mathbf{2.802 \text{ V}}$$

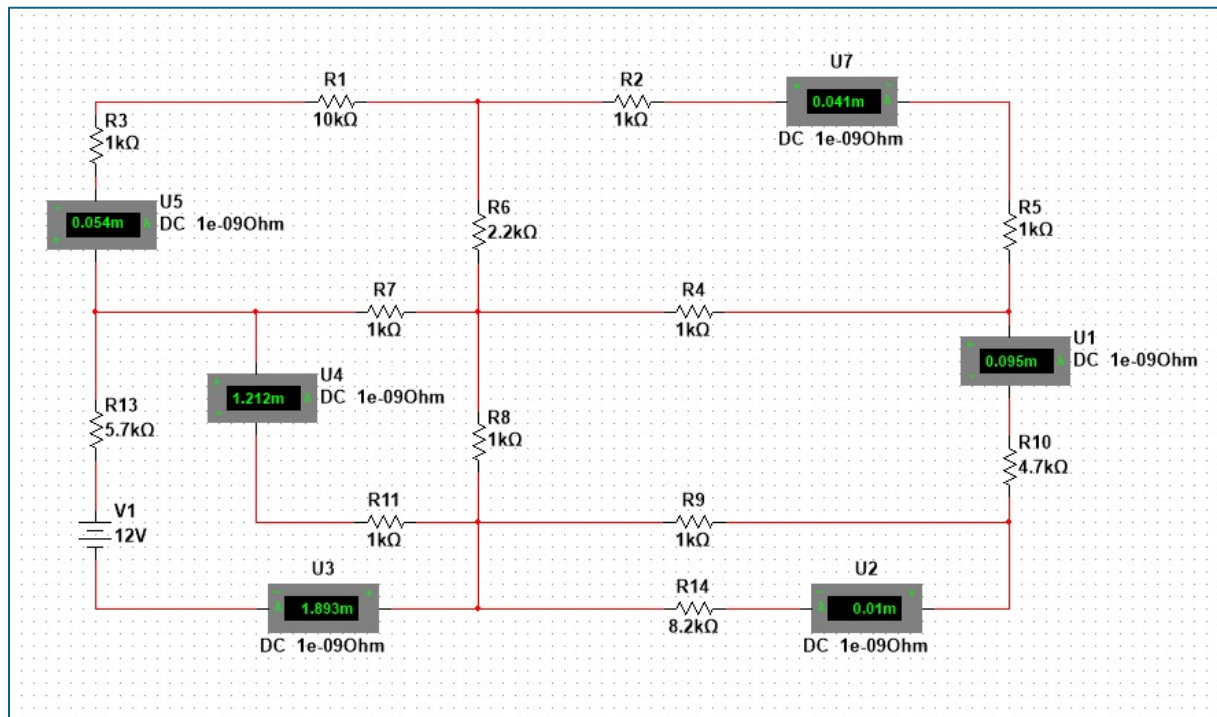2. Calculate and measure the all-loop currents in the figure below.
(Software)



Solution:

Parameter	Theoretical	Experimental	% Error
I₁	0.051 mA	0.053 mA	3.9%
I₂	0.04 mA	0.041 mA	2.5%
I₃	0.093 mA	0.095 mA	2.1%
I₄	0.01 mA	0.01 mA	0
I₅	1.94 mA	1.893 mA	2.4%
I₆	1.2 mA	1.212 mA	1%

Working:

The equations for the six meshes based on Kirchhoff's Voltage Law (KVL) are as follows:

- 1) $12 + 6.7I_1 - I_3 = 0$
- 2) $9.2I_2 - I_4 = 0$
- 3) $8I_3 - I_1 - I_6 = 0$
- 4) $7.7I_4 - I_2 - I_3 - I_5 = 0$
- 5) $5.2I_5 - I_4 - 2.2I_6 = 0$
- 6) $14.2I_6 - 2.2I_5 - I_3 = 0$

A =

$$\begin{bmatrix} 6.7 & 0 & -1 & 0 & 0 & 0 \\ 0 & 9.2 & 0 & -1 & 0 & 0 \\ -1 & 0 & 8 & 0 & 0 & -1 \\ 0 & -1 & -1 & 7.7 & -1 & 0 \\ 0 & 0 & 0 & -1 & 5.2 & -2.2 \\ 0 & 0 & -1 & 0 & -2.2 & 14.2 \end{bmatrix}$$

$$B = [12, 0, 0, 0, 0, 0]^T.$$

Calculated determinants:

$$|A| = 55627.9744$$

$$|A_1| = -108029.184$$

$$|A_2| = -8472.884$$

$$|A_3| = -56259.84$$

$$|A_4| = -8688.48$$

$$|A_5| = -3581.856$$

$$|A_6| = -4516.896$$

- $I_1 = |A_1| / |A| = (-108029.184) / 55627.9744 = -1.94 \text{ A}$
- $I_2 = |A_2| / |A| = (-8472.884) / 55627.9744 = -0.1 \text{ A}$
- $I_3 = |A_3| / |A| = (-56259.84) / 55627.9744 = -1.2 \text{ A}$
- $I_4 = |A_4| / |A| = (-8688.48) / 55627.9744 = -0.093 \text{ A}$
- $I_5 = |A_5| / |A| = (-3581.856) / 55627.9744 = -0.04 \text{ A}$
- $I_6 = |A_6| / |A| = (-4516.896) / 55627.9744 = -0.05 \text{ A}$