

**ELECTRICAL ENGINEERING DEPARTMENT  
CALIFORNIA POLYTECHNIC STATE UNIVERSITY**

**EE 112 Electric Circuit Analysis I**

**EXAM 2**

**Winter 2004**


**Name:** \_\_\_\_\_ **Last 4 digits of Student ID:** \_\_\_\_\_

**Section #:** \_\_\_\_\_

1 (6)	2 (6)	3 (6)	4 (7)	Total (25)

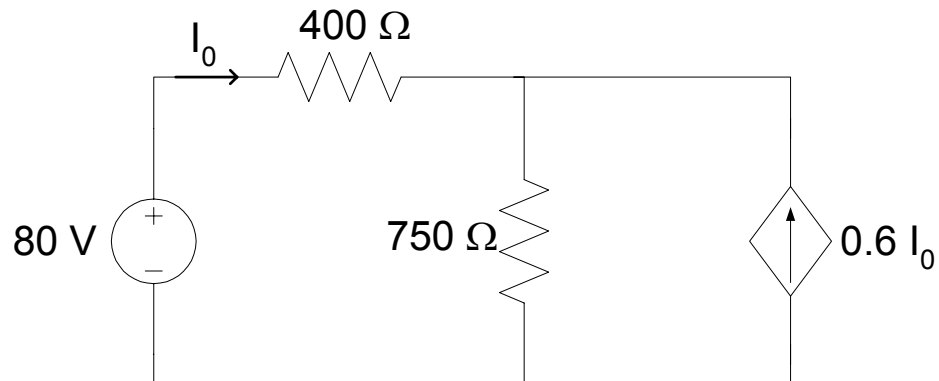
**PROBLEM #1**

Use **Mesh Analysis** to determine the current  $I_0$  in the network shown below.



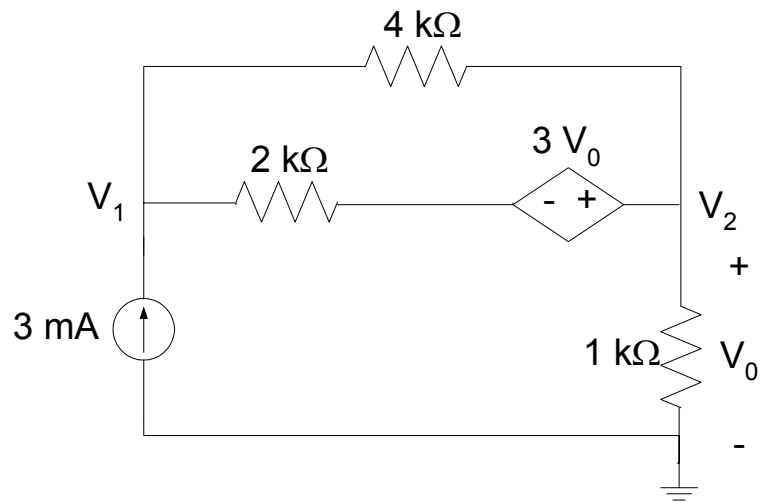PROBLEM #2

For the circuit below, find  $V_1$  and  $V_2$  using **nodal analysis**.




### PROBLEM #3

The mesh equations for the circuit below are

$$\begin{bmatrix} 20 & -40 & -5 \\ -15 & 65 & -25 \\ -5 & -25 & 35 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \\ 0 \end{bmatrix}$$

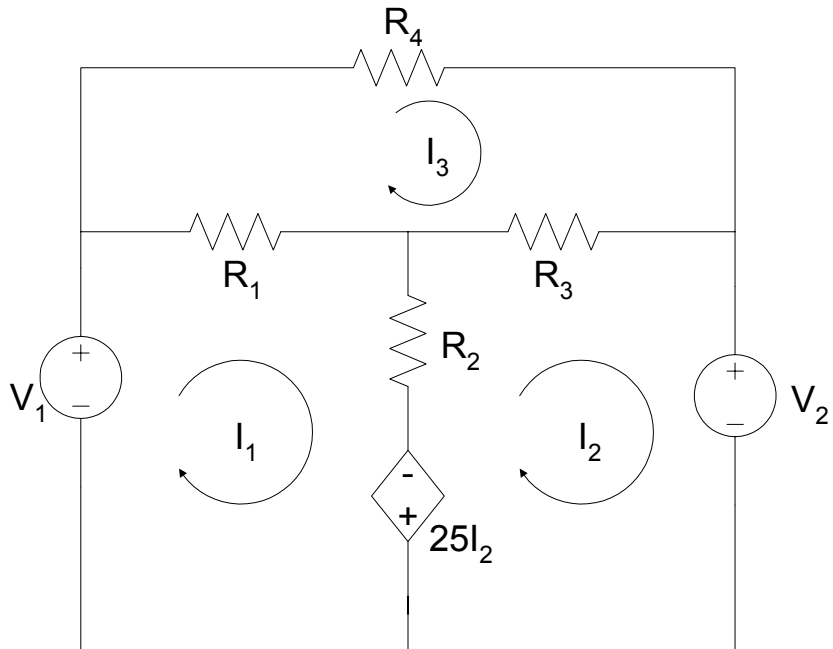Find  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$ .



PROBLEM #4

Using **nodal analysis**, find  $i$ .

