

CS221-L Data Structures and Algorithms Lab



Faculty of Computer Science and Engineering
GIK Institute of Engineering Sciences and Technology

Lab # 12

Shift Registers in Verilog

Submitted by: **Shayan Rizwan Yazdanie [2024585]**

Submitted to: Engr. Irfanullah

Semester: 3rd

Serial-In Serial-Out Shift Register (SISO):

Verilog Code:


```
`timescale 1ns / 1ps
module SISO(input clk, input rst, input din, output dout);
reg [3:0] q;
always @(posedge clk or posedge rst) begin
if (rst)
q <= 4'b0000;
else
q[0] <= q[1];
q[1] <= q[2];
q[2] <= q[3];
q[3] <= din;
end
assign dout = q[3];
endmodule
```

Test Bench

```
`timescale 1ns / 1ps
module SISO_TB();
reg clk, rst, din;
wire dout;
// Instantiate the DUT
SISO uut(.clk(clk), .rst(rst), .din(din), .dout(dout));
always #5 clk = ~clk;
initial begin
// Initialize signals
clk = 0;
rst = 1;
din = 0;
#10;
rst = 0;
din = 1;
#10;
din = 0;
#10;
din = 0;
end
```

```
#10;  
din = 1;  
#10;  
$finish;  
end  
endmodule
```

Output:

 

Serial-In Parallel-Out Shift Register (SIPO):

Verilog Code:

```
`timescale 1ns / 1ps
module SIPO (
input clk,
input rst,
input din,
output reg [3:0] q
);
always @(posedge clk or posedge rst) begin
if (rst)
q <= 4'b0000;
else begin
q[3] <= q[2];
q[2] <= q[1];
q[1] <= q[0];
q[0] <= din;
end
end
endmodule
```

Test Bench


```
`timescale 1ns / 1ps
module tb_SIPO;
reg clk;
reg rst;
reg din;
wire [3:0] q;
// Instantiate DUT
SIPO uut ( .clk(clk), .rst(rst),
.din(din),
.q(q)
initial begin
clk = 0;
forever #5 clk = ~clk;
end
initial begin
rst = 1;
din = 0;
#10;
```

```

rst = 0;
din = 1; #10; // Bit 1
din = 0; #10; // Bit 2
din = 1; #10; // Bit 3
din = 1; #10; // Bit 4
din = 0; #10;
din = 1; #10;
$finish;
end
endmodule

```

Output:

 

Universal Shift Register (USR):

Verilog Code:

```
`timescale 1ns / 1ps
module universal_SR (
input clk, rst, input [1:0] mode, input SI_left,
input SI_right, input [3:0] D,
output reg [3:0] Q);
always @(posedge clk) begin
if (rst) begin
Q[3] <= 0;
Q[2] <= 0;
Q[1] <= 0;
Q[0] <= 0;
end
else begin
case(mode)
2'b00: begin // HOLD
// Do nothing
end
2'b01: begin // SHIFT RIGHT
Q[3] <= SI_left;
Q[2] <= Q[3];
Q[1] <= Q[2];
Q[0] <= Q[1];
end
2'b10: begin // SHIFT LEFT
Q[3] <= Q[2];
Q[2] <= Q[1];
Q[1] <= Q[0];
Q[0] <= SI_right;
end
2'b11: begin // PARALLEL LOAD
Q[3] <= D[3];
Q[2] <= D[2];
Q[1] <= D[1];
Q[0] <= D[0];
end
endcase
end
endcase
```

```
end  
end  
endmodule
```

Test Bench

```
`timescale 1ns / 1ps  
module universal_SR_TB;  
reg clk;  
reg rst;  
reg [1:0] mode;  
reg SI_left;  
reg SI_right;  
reg [3:0] D;  
wire [3:0] Q;  
universal_SR uut (  
    .clk(clk),  
    .rst(rst),  
    .mode(mode),  
    .SI_left(SI_left),  
    .SI_right(SI_right),  
    .D(D),  
    .Q(Q)  
);  
initial begin  
    clk = 0;  
    forever #5 clk = ~clk;  
end  
initial begin  
    // Initialize inputs  
    rst = 1;  
    mode = 2'b00;  
    SI_left = 0;  
    SI_right = 0;  
    D = 4'b0000;  
    #10;  
    rst = 0;  
    #10;  
    mode = 2'b11;  
    D = 4'b1010;  
    #10;  
    mode = 2'b00;  
    #10;  
    mode = 2'b01;
```

```

SI_left = 1;
#40;
mode = 2'b10;
SI_right = 0;
#40;
mode = 2'b00;
#10;
$finish;
end
endmodule

```

Output:

