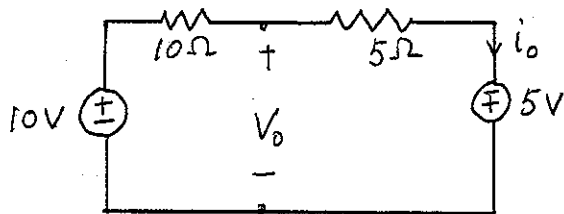


Section: \_\_\_\_\_

Name: \_\_\_\_\_

Last 4 digits of ID: \_\_\_\_\_

1. Find  $i_o$  and  $V_o$  in the circuit below.



2. Find  $V_o$  and the voltage across the current sources.

